 


Summary: Defining a module

- A module is the main building block in Verilog
- We first need to declare:
 - Name of the module
 - Types of its connections (input, output)
 - Names of its connections



Summary: Defining a module



```
module example (a, b, c, y);  
    input a;  
    input b;  
    input c;  
    output y;  
  
    // here comes the circuit description  
  
endmodule
```

Summary: What if we have busses ?

- You can also define multi-bit busses.


- [range_start : range_end]

```
input  [31:0] a; // a[31], a[30] .. a[0]
output [15:8] b1; // b1[15], b1[14] .. b1[8]
output [7:0]  b2; // b2[7], b2[6] .. b1[0]
input          clk;
```

Structural HDL Example

Short Instantiation
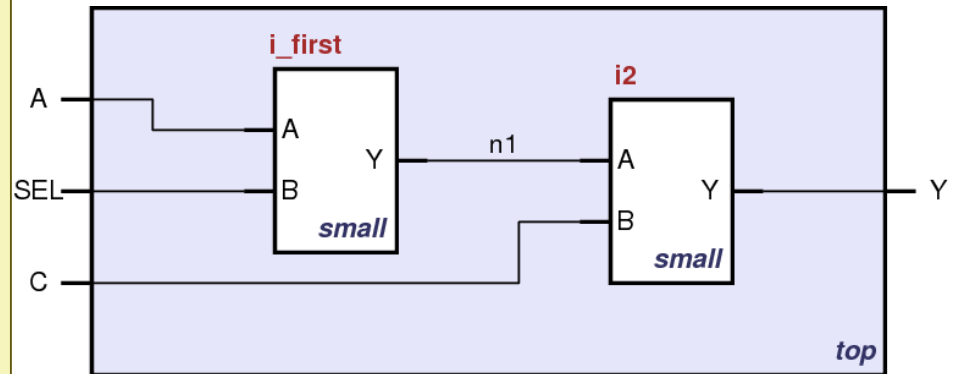
```
module top (A, SEL, C, Y);  
  input A, SEL, C;  
  output Y;  
  wire n1;  
  
  // alternative  
  small i_first ( A, SEL, n1 );  
  
  /* Shorter instantiation,  
     pin order very important */  
  
  // any pin order, safer choice  
  small i2 ( .B(C),  
             .Y(Y),  
             .A(n1) );  
  
endmodule
```



```
module small (A, B, Y);  
  input A;  
  input B;  
  output Y;  
  
  // description of small  
  
endmodule
```

Summary: Bitwise Operators

```
module gates(input [3:0] a, b,  
             output [3:0] y1, y2, y3, y4, y5);  
  
    /* Five different two-input logic  
       gates acting on 4 bit busses */  
  
    assign y1 = a & b;      // AND  
    assign y2 = a | b;      // OR  
    assign y3 = a ^ b;      // XOR  
    assign y4 = ~(a & b);   // NAND  
    assign y5 = ~(a | b);   // NOR  
  
endmodule
```

Summary: Conditional Assignment

- **? :** is also called a **ternary operator** because it operates on 3 inputs:
 - s
 - d1
 - d0.

```
module mux2(input [3:0] d0, d1,  
            input      s,  
            output [3:0] y);  
  
    assign y = s ? d1 : d0;  
    // if (s) then y=d1 else y=d0;  
  
endmodule
```

Summary: How to Express numbers ?

N’ **B****xx**

8’ **b****0000_0001**

■ **(N) Number of bits**

- Expresses how many bits will be used to store the value

■ **(B) Base**

- Can be b (binary), h (hexadecimal), d (decimal), o (octal)

■ **(xx) Number**

- The value expressed in base, apart from numbers it can also have X and Z as values.
- Underscore _ can be used to improve readability

Summary: Verilog Number Representation

Verilog	Stored Number	Verilog	Stored Number
4'b1001	1001	4'd5	0101
8'b1001	0000 1001	12'hFA3	1111 1001 0011
8'b0000_1001	0000 1001	8'o12	00 001 010
8'bxX0X1zZ1	XX0X 1ZZ1	4'h7	0111
'b01	0000 .. 0001	12'h0	0000 0000 0000

Precedence of Operations in Verilog

Highest	~	NOT
	*, /, %	mult, div, mod
	+, -	add,sub
	<<, >>	shift
	<<<, >>>	arithmetic shift
	<, <=, >, >=	comparison
	==, !=	equal, not equal
	&, ~&	AND, NAND
	^, ~^	XOR, XNOR
	, ~	OR, NOR
Lowest	?:	ternary operator

Sequential Logic in Verilog

- **Define blocks that have memory**
 - Flip-Flops, Latches, Finite State Machines
- **Sequential Logic is triggered by a 'CLOCK' event**
 - Latches are sensitive to level of the signal
 - Flip-flops are sensitive to the transitioning of clock
- **Combinational constructs are not sufficient**
 - We need new constructs:
 - `always`
 - `initial`


always Statement, Defining Processes

```
always @ (sensitivity list)  
    statement;
```

- Whenever the event in the sensitivity list occurs, the statement is executed

 Example: D Flip-Flop

```
module flop(input          clk,  
            input    [3:0] d,  
            output reg [3:0] q);  
  
    always @ (posedge clk)  
        q <= d;                // pronounced “q gets d”  
  
endmodule
```



Example: D Flip-Flop

```
module flop(input          clk,  
            input    [3:0] d,  
            output reg [3:0] q);  
  
    always @ (posedge clk)  
        q <= d;                // pronounced “q gets d”  
  
endmodule
```

- The posedge defines a rising edge (transition from 0 to 1).
- This process will trigger only if the **clk signal rises**.
- Once the clk signal rises: the value of **d** will be copied to **q**

Example: D Flip-Flop

```
module flop(input          clk,  
            input    [3:0] d,  
            output reg [3:0] q);  
  
    always @ (posedge clk)  
        q <= d;                // pronounced “q gets d”  
  
endmodule
```

- **‘assign’ statement is not used within always block**
- **The <= describes a ‘non-blocking’ assignment**
 - We will see the difference between ‘blocking assignment’ and ‘non-blocking’ assignment in a while

Example: D Flip-Flop

```
module flop(input          clk,  
            input [3:0] d,  
            output reg [3:0] q);  
  
    always @ (posedge clk)  
        q <= d;                // pronounced “q gets d”  
  
endmodule
```

- Assigned variables need to be declared as **reg**
- The name reg does not necessarily mean that the value is a register. (It could be, it does not have to be).
- We will see examples later

D Flip-Flop with Asynchronous Reset

```
module flop_ar (input          clk,
                input          reset,
                input    [3:0] d,
                output reg [3:0] q);

  always @ (posedge clk, negedge reset)
  begin
    if (reset == '0') q <= 0;    // when reset
    else               q <= d;    // when clk
  end
endmodule
```

- In this example: two events can trigger the process:
 - A *rising edge* on clk
 - A *falling edge* on reset

D Flip-Flop with Asynchronous Reset

```
module flop_ar (input          clk,
                input          reset,
                input [3:0] d,
                output reg [3:0] q);

  always @ (posedge clk, negedge reset)
    begin
      if (reset == '0') q <= 0;    // when reset
      else               q <= d;    // when clk
    end
endmodule
```

- For longer statements a begin end pair can be used
 - In this example it was not necessary
- The always block is *highlighted*

D Flip-Flop with Asynchronous Reset

```
module flop_ar (input          clk,
                input          reset,
                input [3:0] d,
                output reg [3:0] q);

    always @ (posedge clk, negedge reset)
    begin
        if (reset == '0') q <= 0; // when reset
        else               q <= d; // when clk
    end
endmodule
```

- **First reset is checked, if reset is 0, q is set to 0.**
 - This is an 'asynchronous' reset as the reset does not care what happens with the clock
- **If there is no reset then normal assignment is made**

D Flip-Flop with Synchronous Reset

```
module flop_sr (input          clk,
                input          reset,
                input  [3:0] d,
                output reg [3:0] q);

  always @ (posedge clk)
  begin
    if (reset == '0') q <= 0;    // when reset
    else               q <= d;    // when clk
  end
endmodule
```

- The process is only sensitive to clock
 - Reset *only happens* when the *clock rises*. This is a 'synchronous' reset
- A small change, has a large impact on the outcome

D Flip-Flop with Enable and Reset


```
module flop_ar (input          clk,
                input          reset,
                input          en,
                input [3:0] d,
                output reg [3:0] q);

    always @ (posedge clk. negedge reset)
    begin
        if (reset == '0') q <= 0;    // when reset
        else if (en)      q <= d;    // when en AND clk
    end
endmodule
```

- A flip-flop with enable and reset
 - Note that the en signal is **not** in the sensitivity list
- Only when “clk is rising” **AND** “en is 1” data is stored

 Example: D Latch

```
module latch (input          clk,  
              input    [3:0] d,  
              output reg [3:0] q);  
  
  always @ (clk, d)  
    if (clk) q <= d;      // latch is transparent when  
                          // clock is 1  
  
endmodule
```



Summary: Sequential Statements so far

- Sequential statements are within an **'always'** block
- The sequential block is triggered with a change in the sensitivity list
- Signals assigned within an always must be declared as **reg**
- We use **<=** for (non-blocking) assignments and do not use **'assign'** within the always block.

Summary: Basics of always Statements

```
module example (input          clk,
                 input    [3:0] d,
                 output reg [3:0] q);

    wire [3:0] normal;           // standard wire
    reg  [3:0] special;          // assigned in always

    always @ (posedge clk)
        special <= d;            // first FF array

    assign normal = ~ special; // simple assignment

    always @ (posedge clk)
        q <= normal;             // second FF array
endmodule
```

- You can have many always blocks

Summary: Basics of always Statements

```
module example (input          clk,
                 input    [3:0] d,
                 output reg [3:0] q);

    wire [3:0] normal;           // standard wire
    reg  [3:0] special;          // assigned in always

    always @ (posedge clk)
        special <= d;            // first FF array

    assign normal = ~ special;    // simple assignment

    always @ (posedge clk)
        q <= normal;             // second FF array
endmodule
```

- Assignments are different within always blocks

Why does an always Statement Memorize?

```
module flop (input          clk,  
             input    [3:0] d,  
             output reg [3:0] q);  
  
    always @ (posedge clk)  
        begin  
            q <= d;    // when clk rises copy d to q  
        end  
endmodule
```

- This statement describes what happens to signal q
- ... but what happens when clock is not rising?

Why does an always Statement Memorize?

```
module flop (input          clk,  
             input    [3:0] d,  
             output reg [3:0] q);  
  
    always @ (posedge clk)  
        begin  
            q <= d;    // when clk rises copy d to q  
        end  
endmodule
```

- This statement describes what happens to signal q
- ... but what happens when clock is not rising?
- The value of q is preserved (memorized)

Why does an always Statement Memorize?

```
module comb (input          inv,
              input    [3:0] data,
              output reg [3:0] result);

  always @ (inv, data)      // trigger with inv, data
    if (inv) result <= ~data; // result is inverted data
    else   result <= data;   // result is data

endmodule
```

- **This statement describes what happens to signal result**
 - When inv is 1, result is ~data
 - What happens when inv is **not 1** ?

Why does an always Statement Memorize?

```
module comb (input          inv,
              input    [3:0] data,
              output reg [3:0] result);

  always @ (inv, data)          // trigger with inv, data
    if (inv) result <= ~data; // result is inverted data
    else    result <= data;  // result is data

endmodule
```

- **This statement describes what happens to signal result**

- When inv is 1, result is ~data
- When inv is not 1, result is data

- **Circuit is combinational (no memory)**

- The output (result) is defined for all possible inputs (inv data)

always Blocks for Combinational Circuits

- If the statements define the signals completely, nothing is memorized, block becomes combinational.
 - Care must be taken, it is easy to make mistakes and unintentionally describe memorizing elements (latches).
- Always blocks allow powerful statements
 - `if .. then .. else`
 - `case`
- Use always blocks only if it makes your job easier

Always Statement is not Always Practical...

```
reg [31:0] result;
wire [31:0] a, b, comb;
wire      sel,

always @ (a, b, sel)    // trigger with a, b, sel
    if (sel) result <= a; // result is a
    else      result <= b; // result is b

assign comb = sel ? a : b;

endmodule
```

- Both statements describe the same multiplexer
- In this case, the always block is more work

Sometimes Always Statements are Great

```
module sevensegment (input      [3:0] data,
                     output reg [6:0] segments);

    always @ ( * )                // * is short for all signals
    case (data)                    // case statement
        0: segments = 7'b111_1110; // when data is 0
        1: segments = 7'b011_0000; // when data is 1
        2: segments = 7'b110_1101;
        3: segments = 7'b111_1001;
        4: segments = 7'b011_0011;
        5: segments = 7'b101_1011;
        // etc etc
        default: segments = 7'b000_0000; // required
    endcase

endmodule
```

The case Statement

- Like **if .. then .. else** can only be used in always blocks
- The result is combinational only if the output is defined for all cases
 - Did we mention this before ?
- Always use a **default** case to make sure you did not forget a case (which would infer a latch)
- Use **casez** statement to be able to check for don't cares
 - See book page 202, example 4.28

Non-blocking and Blocking Statements

Non-blocking

```
always @ (a)
begin
    a <= 2'b01;
    b <= a;
    // all assignments are made here
    // b is not (yet) 2'b01
end
```

- Values are assigned at the end of the block.
- All assignments are made in parallel, process flow is **not-blocked**.

Blocking

```
always @ (a)
begin
    a = 2'b01;
    // a is 2'b01
    b = a;
    // b is now 2'b01 as well
end
```

- Value is assigned immediately.
- Process waits until the first assignment is complete, it **blocks** progress.

Why use (Non)-Blocking Statements

- **There are technical reasons why both are required**
 - It is out of the scope of this course to discuss these
- **Blocking statements allow sequential descriptions**
 - More like a programming language
- **If the sensitivity list is correct, blocks with non-blocking statements will always evaluate to the same result**
 - It may require some additional iterations

Example: Blocking Statements

- Assume all inputs are initially '0'

```
always @ ( * )  
begin  
    p    = a ^ b ;           // p    = 0  
    g    = a & b ;           // g    = 0  
    s    = p ^ cin ;         // s    = 0  
    cout = g | (p & cin) ;   // cout = 0  
end
```

Example: Blocking Statements

- Now **a** changes to '1'

```
always @ ( * )  
begin  
    p    = a ^ b ;           // p    = 1  
    g    = a & b ;           // g    = 0  
    s    = p ^ cin ;        // s    = 1  
    cout = g | (p & cin) ;  // cout = 0  
end
```

- The process triggers
- All values are updated in order
- At the end, **s = 1**

Same Example: Non-Blocking Statements

- Assume all inputs are initially '0'

```
always @ ( * )  
begin  
    p    <= a ^ b ;           // p    = 0  
    g    <= a & b ;           // g    = 0  
    s    <= p ^ cin ;        // s    = 0  
    cout <= g | (p & cin) ;  // cout = 0  
end
```

Same Example: Non-Blocking Statements

- Now **a** changes to '1'

```
always @ ( * )  
begin  
    p    <= a ^ b ;           // p    = 1  
    g    <= a & b ;           // g    = 0  
    s    <= p ^ cin ;        // s    = 0  
    cout <= g | (p & cin) ;   // cout = 0  
end
```

- The process triggers
- All assignments are concurrent
- When **s** is being assigned, **p** is still 0, result is still 0

Same Example: Non-Blocking Statements

- After the first iteration **p** has changed to '1' as well

```
always @ ( * )  
begin  
    p    <= a ^ b ;           // p    = 1  
    g    <= a & b ;           // g    = 0  
    s    <= p ^ cin ;        // s    = 1  
    cout <= g | (p & cin) ;   // cout = 0  
end
```

- Since there is a change in **p**, process triggers again
- This time **s** is calculated with **p=1**
- The result is correct after the second iteration

Rules for Signal Assignment

- Use **always @(posedge clk)** and non-blocking assignments (**<=**) to model synchronous sequential logic

```
always @ (posedge clk)
    q <= d; // nonblocking
```

- Use continuous assignments (**assign ...**) to model simple combinational logic.

```
assign y = a & b;
```


Rules for Signal Assignment (cont)

- Use **always @ (*)** and blocking assignments **(=)** to model more complicated combinational logic where the always statement is helpful.
- Do not make assignments to the same signal in more than one always statement or continuous assignment statement