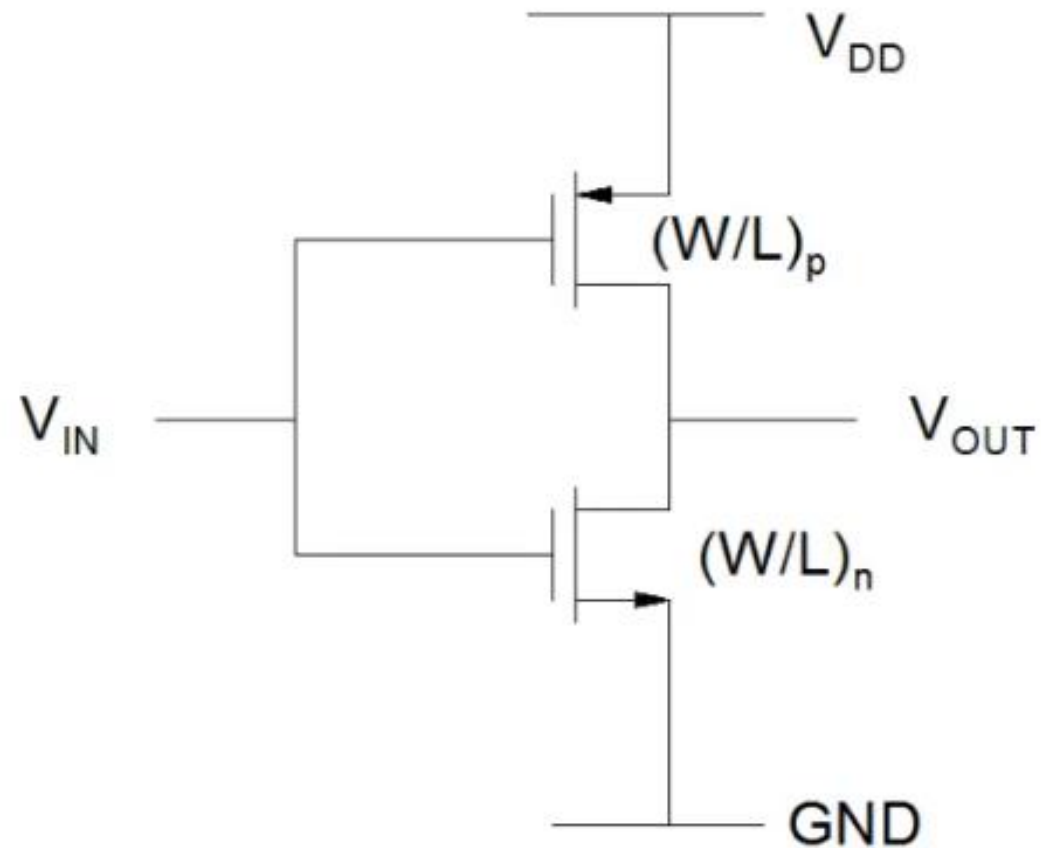


Logic "1" is V_{DD} and "logic 0" is GND independent of size of transistors.



There is "no" static power dissipation in the circuit

CMOS Inverter



How should we size to obtain symmetrical VTC ?

CMOS Inverter : VTC

  

Both NMOS and PMOS are in saturation region

CMOS Inverter : VTC

$$I_{DSN} = I_{SDP}$$

$$\frac{\beta_N}{2}(V_{inv} - V_{THN})^2 = \frac{\beta_P}{2}(V_{SGP} + V_{THP})^2$$


$$V_{SGP} = V_{DD} - V_{inv}$$

$$\beta_N = W_N/L_N KP_N$$

$$\beta_P = W_P/L_P KP_P$$

$$V_{INV} = \frac{V_{THN} + \frac{1}{\sqrt{\beta_R}}(V_{DD} + V_{THP})}{1 + \frac{1}{\sqrt{\beta_R}}}$$
 
$$\beta_R = \frac{\beta_N}{\beta_P} = \left(\frac{W_N/L_N}{W_P/L_P} \right) \times \left(\frac{KP_N}{KP_P} \right)$$



CMOS Inverter : VTC


$$V_{INV} = \frac{V_{THN} + \frac{1}{\sqrt{\beta_R}}(V_{DD} + V_{THP})}{1 + \frac{1}{\sqrt{\beta_R}}}$$


$$V_{INV} = 0.5V_{DD}$$

$$\beta_R = \frac{0.5V_{DD} + V_{THP}}{0.5V_{DD} - V_{THN}}$$

$$\Rightarrow \beta_R = 1$$
 
$$\frac{W_P/L_P}{W_N/L_N} = \frac{KP_N}{KP_P} \quad 2.0$$



 


$$V_{IL} = 1.48V; v_{ol} = 0V$$

$$V_{IH} = 1.814V; v_{oh} = 3.3V$$

$$NM_H = 1.48V; NM_L = 1.48V$$

$$\frac{NM_H}{0.5V_{DD}} = 0.9$$

CMOS Inverter : V_{IH} ; V_{IL}

 

At V_{IL} , PMOS in Linear and NMOS in Saturation

CMOS Inverter : V_{IH} ; V_{IL}





W_P/W_N	V_{INV}	V_{IH}	V_{IL}	V_{OH}	V_{OL}
1	1.53	1.67	1.34	3.16	0.177
2	1.65	1.81	1.48	3.14	0.166
3	1.7	1.9	1.575	3.12	0.148

CMOS Inverter : V_{IL}

$$\frac{\beta_N}{2}(V_{IL} - V_{THN})^2 = \beta_P((V_{DD} - V_{IL} + V_{THP})(V_{DD} - V_{OUT}) - 0.5(V_{DD} - V_{OUT})^2)$$

- Gain of inverter is Unity

CMOS Inverter : V_{IH} ; V_{IL}

 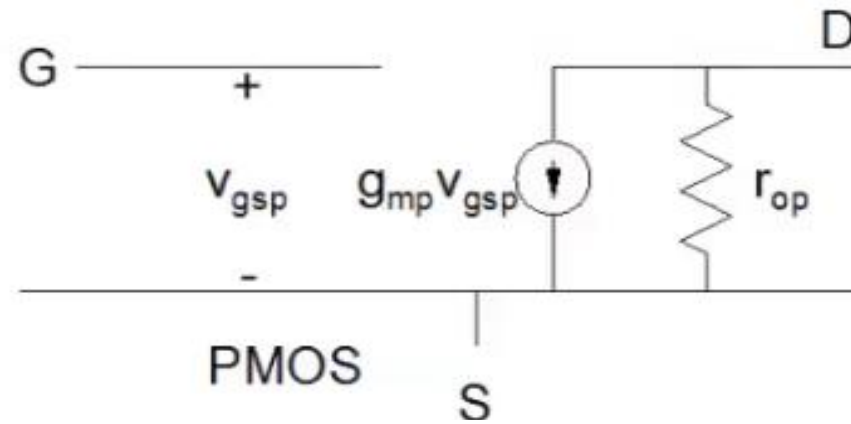  

$$G = -(g_{MN} + g_{MP}) \times r_{ON} \parallel r_{OP}$$

CMOS Inverter : V_{IL}

$$G = -(g_{MN} + g_{MP}) \times r_{ON} \parallel r_{OP} = -1$$



$$\Rightarrow (g_{MN} + g_{MP}) \times r_{OP} \cong 1$$

$$g_{mn} = \beta_N \times (V_{IL} - V_{THN}) ; g_{mp} = \beta_P \times (V_{DD} - V_{OUT})$$

$$r_{op} = \frac{1}{\beta_P \times (V_{DD} - V_{IL} + V_{THP} + V_{DD} - V_{OUT})}$$


$$\frac{\beta_N}{2} (V_{IL} - V_{THN})^2 = \beta_P ((V_{DD} - V_{IL} + V_{THP})(V_{DD} - V_{OUT}) - 0.5(V_{DD} - V_{OUT})^2)$$
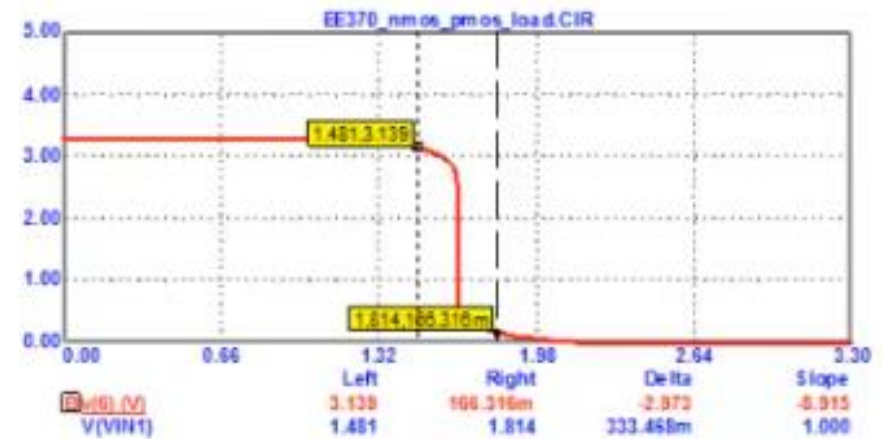 
$$V_{IL} \sim V_{inv} - \delta V ; V_{IH} \sim V_{inv} + \delta V$$





$$\delta V \sim 0.17V$$

CMOS: Propagation Delay

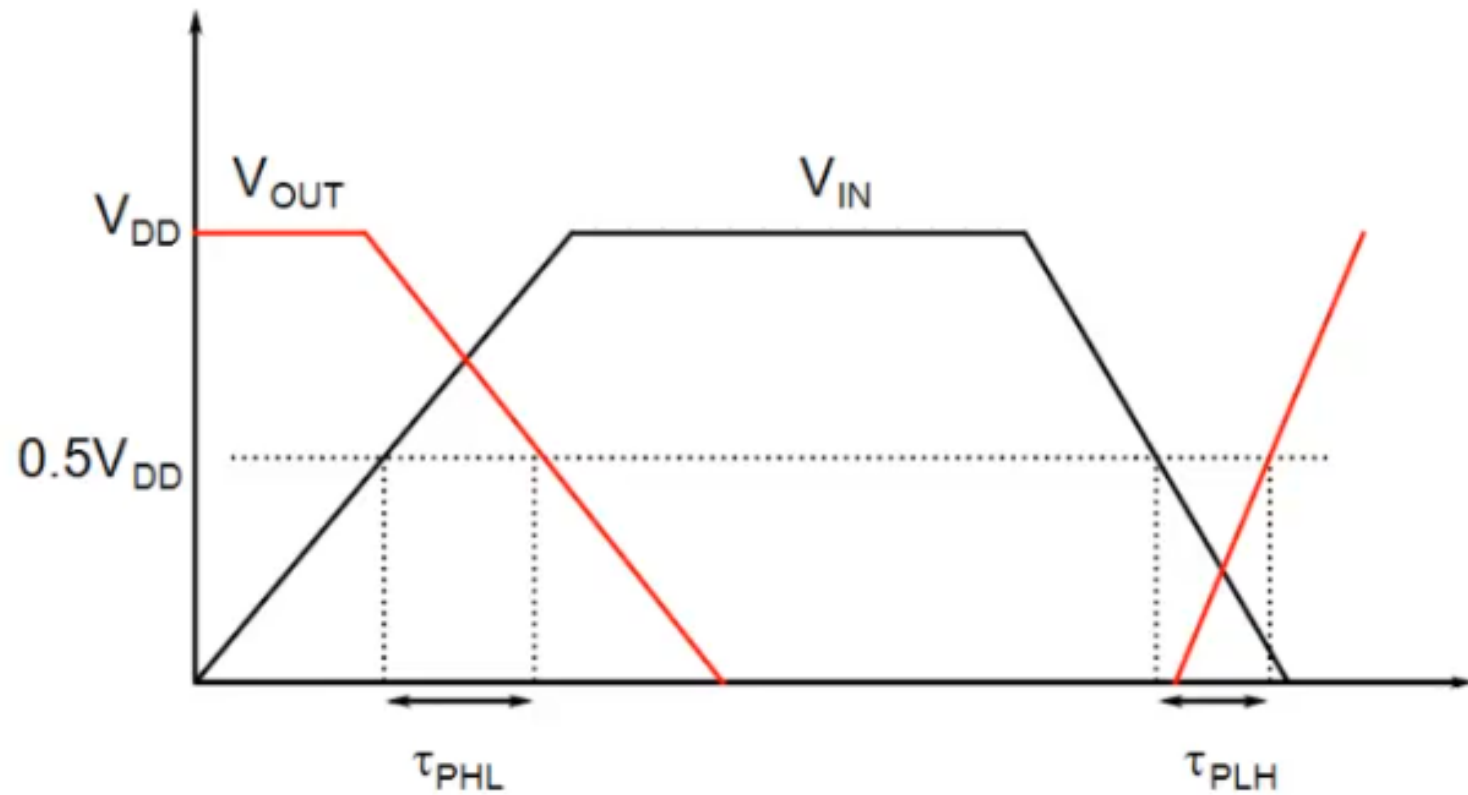

$$\tau_R ; \tau_F ; \tau_{PHL} ; \tau_{PLH}$$


Low to high propagation delay

 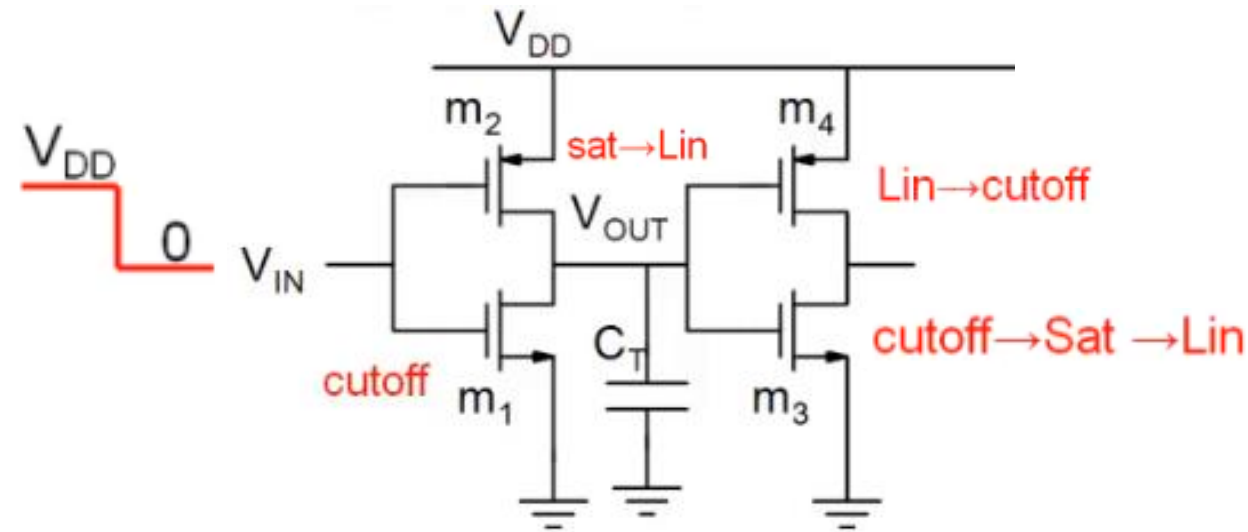

$$\tau_{phl} \cong 0.5 \times \frac{\tilde{C}_T V_{DD}}{\tilde{I}_{pd}}$$

$$\tau_{plh} \cong 0.5 \times \frac{\tilde{C}_T V_{DD}}{\tilde{I}_{pu}}$$
 
$$C_T = (C_{gdn1} + C_{dbn1} + C_{gdp2} + C_{dbp2}) + \\ (C_{gsn3} + C_{gdn3} + C_{gbn3} + C_{gsp4} + C_{gdp4} + C_{gbp4})$$





$$A_{D1} = 4 \times 1 + 6 \times 6 = 40;$$

$$P_{D1} = (1 + 1 + 6) \times 2 + 6 = 22$$

$$A_{D2} = 8 \times 4 + 3 \times 6 = 50;$$
 
$$P_{D2} = (4 + 1 + 3) \times 2 + 6 = 22$$



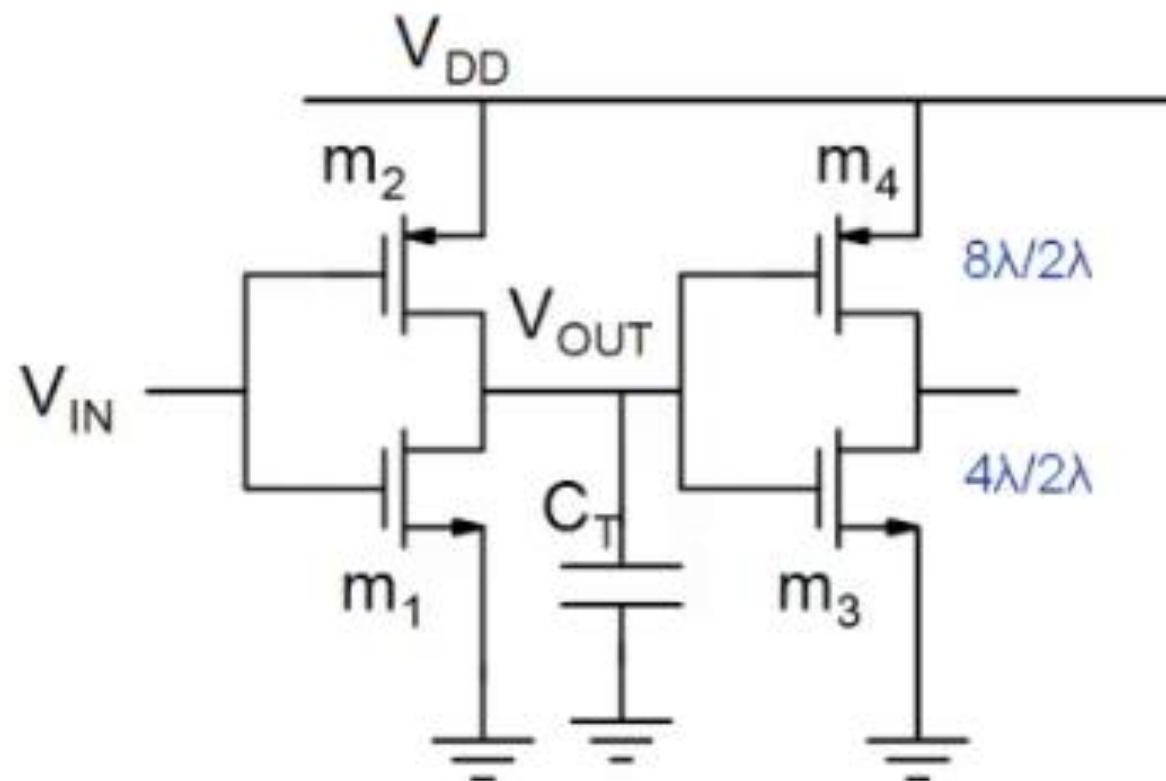


$$C_T = \left(\overset{\sim 0.3\text{fF}}{C_{gdn1}} + \overset{\sim 6\text{fF}}{C_{dbn1}} + \overset{\sim 0.6\text{fF}}{C_{gdp2}} + \overset{\sim 6\text{fF}}{C_{dbp2}} \right) +$$

$$\left(\underbrace{C_{gsn3} + C_{gdn3} + C_{gbn3}}_{\sim 2.0\text{fF}} + \underbrace{C_{gsp4} + C_{gdp4} + C_{gbp43}}_{\sim 5\text{fF}} \right)$$

$$\sim 13+7\text{fF}$$

Delay Analysis :

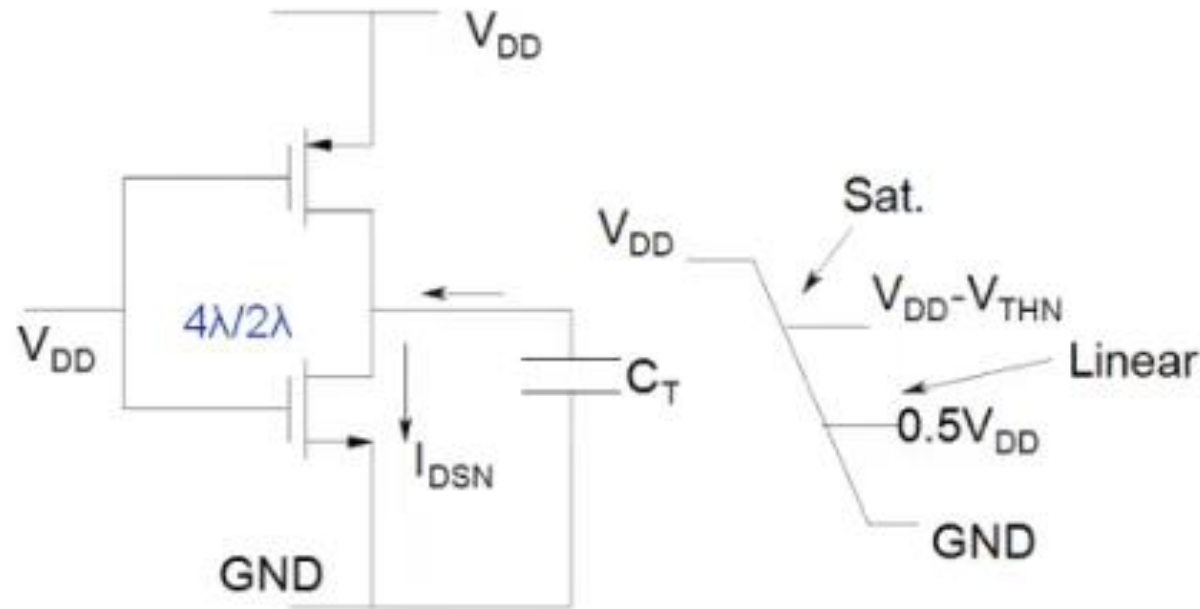

$$\tau_{phl} \cong 0.5 \times \frac{\tilde{C}_T V_{DD}}{\tilde{I}_{pd}} \quad \tau_{phl} \sim 65 ps$$

42+23



$$I_{DS}(t=0) = \left(KP_N \times \frac{W_N}{L_N} \right) \times \frac{(V_{DD} - V_{THN})^2}{2}$$

$$I_{DS}(t = \tau_{phl}) = \left(KP_N \times \frac{W_N}{L_N} \right) \times \left((V_{DD} - V_{THN}) \frac{V_{DD}}{2} - \frac{V_{DD}^2}{8} \right)$$

~0.53mA $\rightarrow \tilde{I}_{pd} \sim 0.5mA$
 ~0.487mA \rightarrow

Delay Analysis :

  
$$\tau_{plh} \cong 0.5 \times \frac{\tilde{C}_T V_{DD}}{\tilde{I}_{pu.}} \quad \tau_{plh} \sim 65 ps$$



$$I_{SDP}(t=0) = \left(KP_P \times \frac{W_P}{L_P} \right) \times \frac{(V_{DD} + V_{THP})^2}{2} \sim 0.53mA$$

$$I_{SDP}(t=\tau_{plh}) = \left(KP_P \times \frac{W_P}{L_P} \right) \times \left((V_{DD} + V_{THP}) \frac{V_{DD}}{2} - \frac{V_{DD}^2}{8} \right) \sim 0.487mA$$


$$\tilde{I}_{pu} \sim 0.5mA$$

 

$$\tau_{phl} \cong 0.5 \times \frac{\tilde{C}_T V_{DD}}{\tilde{I}_{pd.}}$$

$$I_{DS}(t=0) = \left(KP_N \times \frac{W_N}{L_N} \right) \times \frac{(V_{DD} - V_{THN})^2}{2}$$

 
$$I_{DS}(t = \tau_{phl}) = \left(KP_N \times \frac{W_N}{L_N} \right) \times \left((V_{DD} - V_{THN}) \frac{V_{DD}}{2} - \frac{V_{DD}^2}{8} \right)$$




$$\tau_{plh} \cong 0.5 \times \frac{\tilde{C}_T V_{DD}}{\tilde{I}_{pu.}}$$

$$I_{SDP}(t=0) = \left(KP_P \times \frac{W_P}{L_P} \right) \times \frac{(V_{DD} + V_{THP})^2}{2}$$
 
$$I_{SDP}(t = \tau_{plh}) = \left(KP_P \times \frac{W_P}{L_P} \right) \times \left((V_{DD} + V_{THP}) \frac{V_{DD}}{2} - \frac{V_{DD}^2}{8} \right)$$



 

$$\tau_{phl} \cong 0.5 \times \frac{\tilde{C}_T V_{DD}}{\tilde{I}_{pd.}}$$


~13fF

~7fF



$$\tau_{phl} \cong 0.5 \times \frac{\tilde{C}_{in} V_{DD}}{\tilde{I}_{pd.}} + 0.5 \times \frac{\tilde{C}_L V_{DD}}{\tilde{I}_{pd.}}$$

$$\tau_{phl}(ps) \cong 42 + a \times C_L(fF); a = 3.25$$


ps/fF or ns/pF

 

1X Inverter

  

2X Inverter

 

4X Inverter

$$\tau_{phl} (ps) \cong 42 + a \times C_L (fF); a = 1.625$$

$$\tau_{phl} \cong 0.5 \times \frac{\tilde{C}_{in} V_{DD}}{\tilde{I}_{pd.}} + 0.5 \times \frac{\tilde{C}_L V_{DD}}{\tilde{I}_{pd.}}$$



$$\tau_{phl} (ps) \cong 42 + a \times C_L (fF); a = 3.25$$

0.18μm technology, 1.8V VDD

Cell Description


The INV cell provides the logical inversion of a single input (A). The output (Y) is represented by the logic equation:

$$Y = \bar{A}$$

Functions


A	Y
0	1
1	0

Logic Symbol

 

Cell Size

Drive Strength	Height (μm)	Width (μm)
INVXL	5.0	1.3
INVX1	5.0	1.3
INVX2	5.0	2.0
INVX3	5.0	2.6
INVX4	5.0	2.6
INVX8	5.04	3.96
INVX12	5.04	8.58
INVX16	5.04	11.22
INVX20	5.04	12.54

 

$$P_{dynamic} = C_T \times V_{DD}^2 \times f$$

AC Power

Pin	Power (μW/MHz)								
	XL	X1	X2	X3	X4	X8	X12	X16	X20
A	0.0087	0.0114	0.0209	0.0315	0.0378	0.0775	0.1665	0.2250	0.2804


Pin Capacitance

Pin	Capacitance (pF)								
	XL	X1	X2	X3	X4	X8	X12	X16	X20
A	0.0026	0.0036	0.0070	0.0100	0.0129	0.0267	0.0067	0.0088	0.0109

Delays at 25°C, 1.8V, Typical Process


Description	Intrinsic Delay (ns)								
	XL	X1	X2	X3	X4	X8	X12	X16	X20
A → Y↑	0.023	0.023	0.020	0.022	0.018	0.018	0.122	0.119	0.117
A → Y↓	0.015	0.014	0.012	0.013	0.011	0.012	0.119	0.113	0.110

Description	K _{load} (ns/pF)								
	XL	X1	X2	X3	X4	X8	X12	X16	X20
A → Y↑	6.229	4.512	2.256	1.507	1.137	0.519	0.346	0.260	0.208
A → Y↓	3.237	2.401	1.195	0.798	0.598	0.356	0.240	0.180	0.144

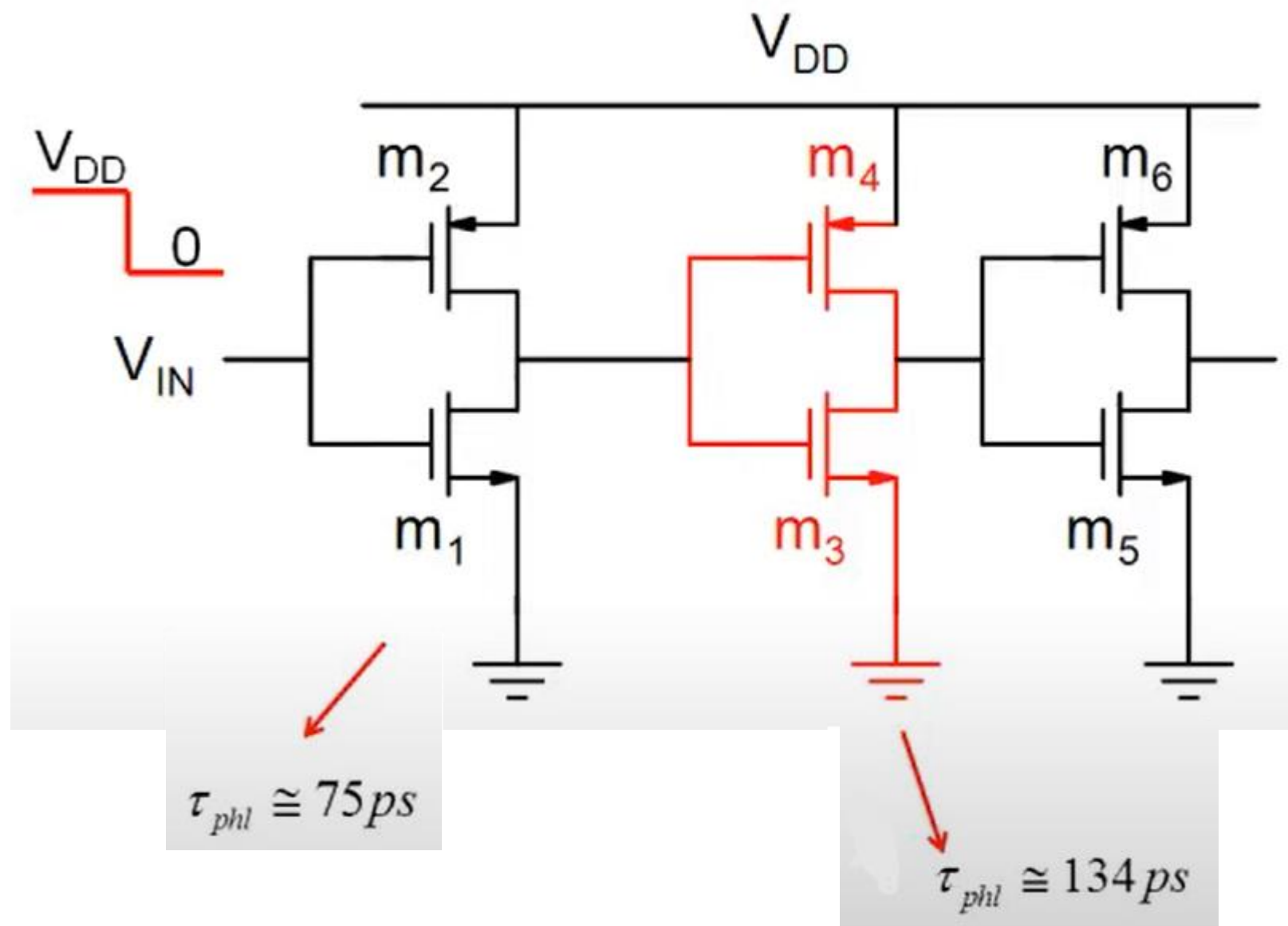

Effect of Input Rise/Fall time
 
$$I_{DSN} - I_{SDP} = -C_T \frac{dV_{OUT}}{dt}$$



- The PMOS does not switch off immediately thereby reducing the discharge current.
- The NMOS does not reach its full current drive capability immediately.

⇒ Propagation delay increases !


Effect of Input Rise/Fall time

Empirical Model :

$$\tau_{PHL} = \sqrt{\tau_{PHLO}^2 + (t_R/2)^2}$$

τ_R / τ_{PHL}	τ_{PHLO} / τ_{PHL}
0.0	1.0
0.5	0.968
1.0	0.866
1.5	0.66

Impact of process variations

 

$$\tau_{phl} \cong 0.5 \times \frac{\tilde{C}_T V_{DD}}{\tilde{I}_{pd.}}$$

$$I_{DS}(t=0) = \left(KP_N \times \frac{W_N}{L_N} \right) \times \frac{(V_{DD} - V_{THN})^2}{2}$$

$$\mu_N C'_{ox}$$

 
 


Fig. 1: Classification of variations. Global variations include (a) lot-to-lot variation (LTLV), (b) wafer-to-wafer variation (WTWV), and (c) die-to-die variation (DTDV). Local variation means (d) within-die variation (WIDV) [1]

Case	NMOS	PMOS
1	nominal	nominal
2	slow	slow
3	slow	fast
4	fast	slow
5	fast	fast


Delay under variations

- Temperatures varying between 0 – 125°C,
- Supply voltage varying between VDD ($\pm 10\%$)
- Process variations of 3σ .

Case	NMOS	PMOS
1	nominal	nominal
2	slow	slow
3	slow	fast
4	fast	slow
5	fast	fast


$$KP_N = 100 \pm 20\%; V_{THN} = 1 \pm 0.1V$$
 
$$KP_P = 50 \pm 20\%; V_{THP} = -1 \pm 0.1V$$




$$V_{IL} = 1.48V; V_{IH} = 1.814V$$

$$N_{ML} = N_{MH} = 1.48V$$

 

$$V_{IL} = 1.3V; V_{IH} = 1.63V$$

$$N'_{ML} = 1.3V; N'_{MH} = 1.3V$$

 

$$V_{IL} = 1.67V; V_{IH} = 2V$$


Delay under variations

- Temperatures varying between 0 – 125°C,
- Supply voltage varying between VDD ($\pm 10\%$)
- Process variations of 3σ .

Case	NMOS	PMOS
1	nominal	nominal
2	slow	slow
3	slow	fast
4	fast	slow
5	fast	fast

Best and Worst Case Delay values

 - Temperatures varying between 0 – 125°C,
- Supply voltage varying between V_{DD} ($1 \pm 10\%$)
- Process variations of 3σ .



Delay Calculation

Using the delay data in the datasheets ($t_{\text{intrinsic}}$, K_{load} , and C_{load}) and the delay derating factors, the estimated total propagation delay is

$$t_{\text{TPD}} = (K_{\text{Process}}) \cdot [1 + (K_{\text{Volt}} \cdot \Delta V_{\text{dd}})] \cdot [1 + (K_{\text{Temp}} \cdot \Delta T)] \cdot t_{\text{typical}}$$

$$t_{\text{typical}} = t_{\text{intrinsic}} + (K_{\text{load}} \cdot C_{\text{load}})$$

where:

t_{TPD} = total propagation delay (ns);

t_{typical} = delay at typical corner—1.8 V, 25°C, typical process (ns);

$t_{\text{intrinsic}}$ = delay through the cell when there is no output load (ns);

K_{load} = load delay multiplier (ns/pF);

C_{load} = total output load capacitance (pF);

K_{Process} = process derating factor, where process is slow, typical, or fast;

K_{Volt} = voltage derating factor (/V);

ΔV_{dd} = $V_{\text{dd}} - 1.8 \text{ V}$;

K_{Temp} = temperature derating factor (/°C);

ΔT = junction temperature — 25°C.

$$\tau_{phl} \cong 0.5 \times \frac{\tilde{C}_T V_{DD}}{\tilde{I}_{pd.}}$$

$$I_{DS}(t=0) = \left(K P_N \times \frac{W_N}{L_N} \right) \times \frac{(V_{DD} - V_{THN})^2}{2}$$

$\mu_N C'_{ox}$

Table 3. Derating Factors

K _{Process} (slow)	1.293
K _{Process} (typical)	1.000 (by definition)
K _{Process} (fast)	0.781
K _{Volt} (1.8V to 1.62V)	-0.731/V
K _{Volt} (1.8V to 1.98V)	-0.511/V

Table 3. Derating Factors

K _{Process} (slow)	1.293
K _{Temp} (25°C to 0°C)	0.00137/°C
K _{Temp} (25°C to 125°C)	0.00123/°C

$$\frac{\tau_{p(\min)}}{\tau_{po}} = 0.78 \times (1 - 0.51 \times 0.18) \times (1 - .00137 \times 25) = 0.68$$

$$\frac{\tau_{p(\max)}}{\tau_{po}} = 1.293 \times (1 + 0.73 \times 0.18) \times (1 + .00123 \times 100) = 1.64$$

Methods for decreasing delay

-Increase the supply voltage

$$\tau_{phl} \cong 0.5 \times \frac{\tilde{C}_T V_{DD}}{\tilde{I}_{pd.}}$$

Supply Voltage	τ_{PHL} (ps)
3.3	75
3.6	65.5
4.0	54.8
5.0	36.6

$$P_{dynamic} = C_T \times V_{DD}^2 \times f$$

$$P_{dynamic} = 0.22 \mu W / MHz$$

$$P_{dynamic} = 0.5 \mu W / MHz$$


Size-

$$\tau_{phl} (ps) \cong \tau_{ins} + a \times C_L (fF); a \propto 1/W_N$$

Power Dissipation

$$P_T = P_{static} + P_{dynamic} + P_{SC}$$


Static power Dissipation

 

- “no” dc path exists between supply and ground under steady state conditions.
- leakage currents, although ‘small’ compared to ON state current, can still be significant .
- Not so true for the state-of-the-art scaled technology nodes
- Leakage power is significant in SOTA Tech. node

-depends on the threshold voltage and increases exponentially as its value is reduced

Dynamic power Dissipation

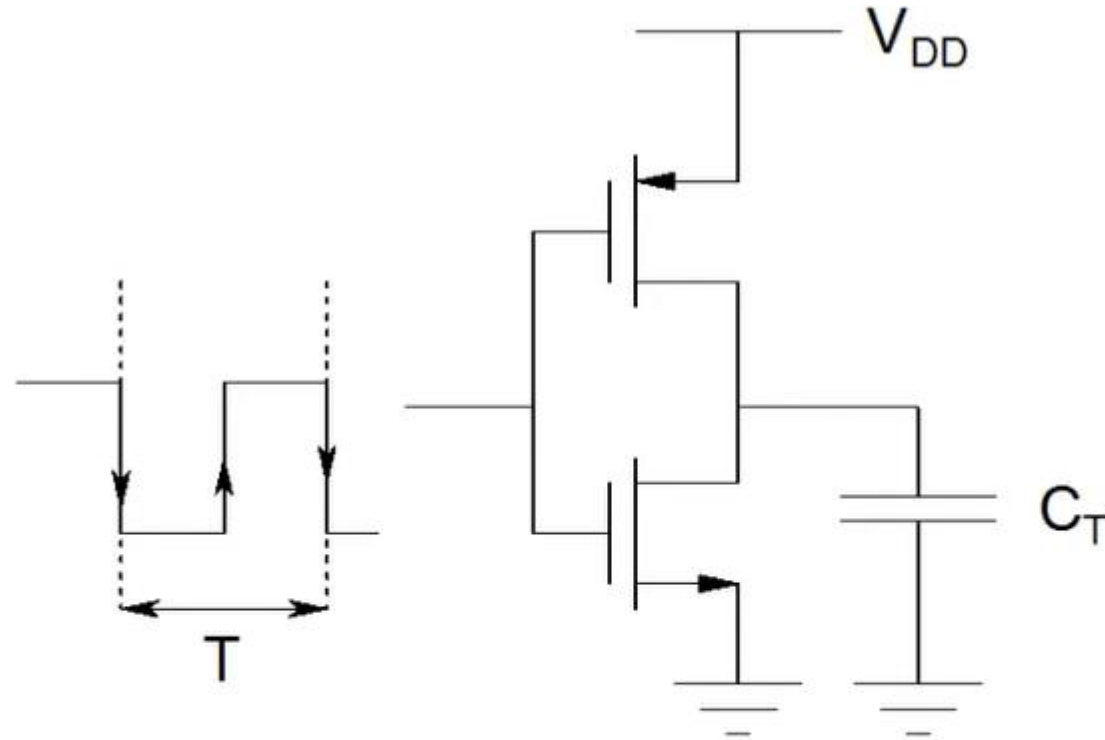


$$E_{Supply} = \int V_{DD} I_{Supply} dt$$

$$I_{Supply} = I_{SDP}$$

$$\int I_{SDP} dt = C_T V_{DD}$$

$$E_{Supply} = C_T V_{DD}^2$$

Dynamic power Dissipation


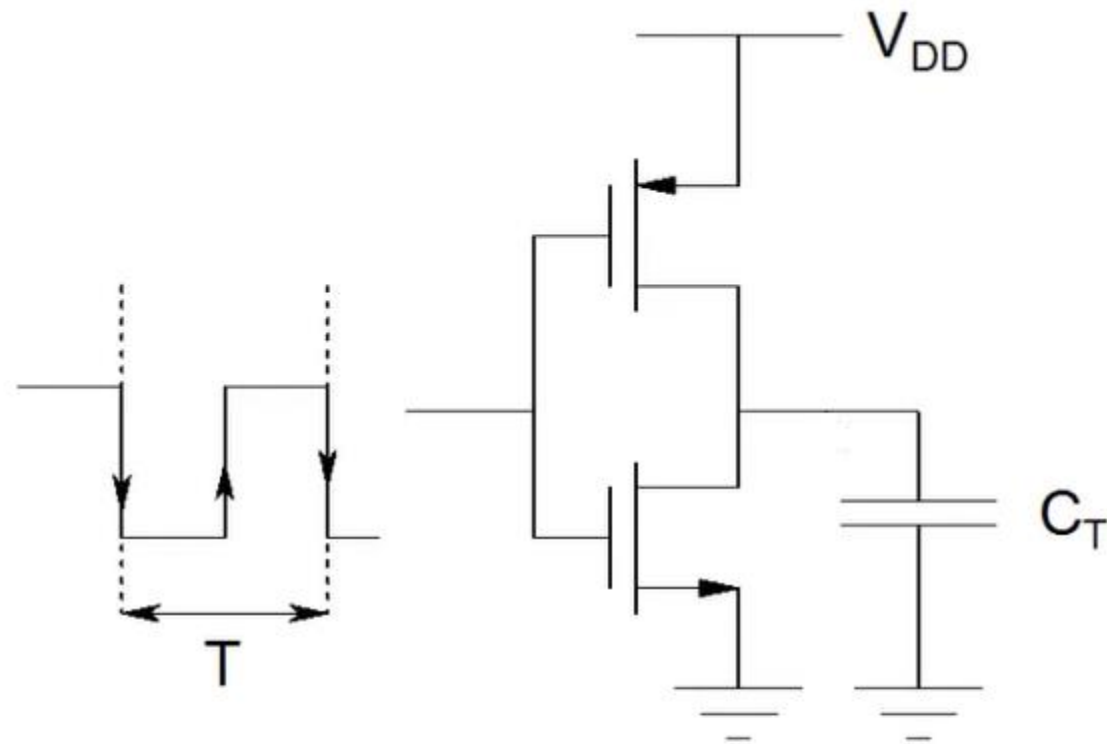


$$E_{Supply} = C_T V_{DD}^2$$

$$E_C = 0.5 \times C_T V_{DD}^2$$

$$P_{dynamic} = f \times C_T \times V_{DD}^2 = 0.22 \mu W / MHz$$

Short-circuit Power Dissipation

  

$$P_{SC} \cong \frac{1}{2} I_{Peak} \frac{(\tau_R + \tau_F)}{T} V_{DD}$$

- Therefore, a small rise and fall time is advantageous from both power as well as delay viewpoints

$$I_{peak} = \left(KP_N \times \frac{W_N}{L_N} \right) \times \frac{(0.5V_{DD} - V_{THN})^2}{2} = 42.25 \mu A$$

$$P_{SC} \cong \frac{1}{2} I_{Peak} \frac{(\tau_R + \tau_F)}{2T} V_{DD} = 0.007 \mu W / MHz$$

for $\tau_R = \tau_F = 0.1 ns$


Power Reduction techniques

- Reducing the supply voltage:

(This however, increases the propagation delay.
could be countered through reduction in threshold
voltage.)

- Reduce the nodal capacitance through layout techniques.
- Reduce the switching activity of nodes

CMOS Inverter : Summary

 


$$V_{INV} = \frac{V_{THN} + \frac{1}{\sqrt{\beta_R}}(V_{DD} + V_{THP})}{1 + \frac{1}{\sqrt{\beta_R}}}$$

$$V_{INV} = 1.65V; V_{IL} = 1.48V; v_{ol} = 0V$$

$$V_{IH} = 1.814V; v_{oh} = 3.3V$$

$$NM_H = 1.48V; NM_L = 1.48V$$


$$A = 28 \times 40 = 1120\lambda^2$$

 

$$A_{DN} = 40; P_{DN} = 22$$

$$A_{DP} = 50; P_{DP} = 22$$
 
$$P_{dynamic} = f \times C_T \times V_{DD}^2 = 0.22\mu W / MHz$$




$$\tau_{phl}(ps) \cong 42 + a \times C_L(fF); a = 3.25$$

$$\tau_{phl} \cong 0.5 \times \frac{\tilde{C}_T V_{DD}}{I_{pd}}$$


$$C_T = (\underbrace{C_{gdn1} + C_{dbn1} + C_{gdp2} + C_{dbp2}}_{\sim 2.0fF} + \underbrace{C_{gsn3} + C_{gdn3} + C_{gbn3} + C_{gsp4} + C_{gdp4} + C_{gbp4}}_{\sim 5fF}) + \dots \sim 13 + 7fF$$

Impact of input rise/fall time

 


$$\tau_{PHL} = \sqrt{\tau_{PHLO}^2 + (t_R/2)^2}$$




2-input CMOS NAND Gate

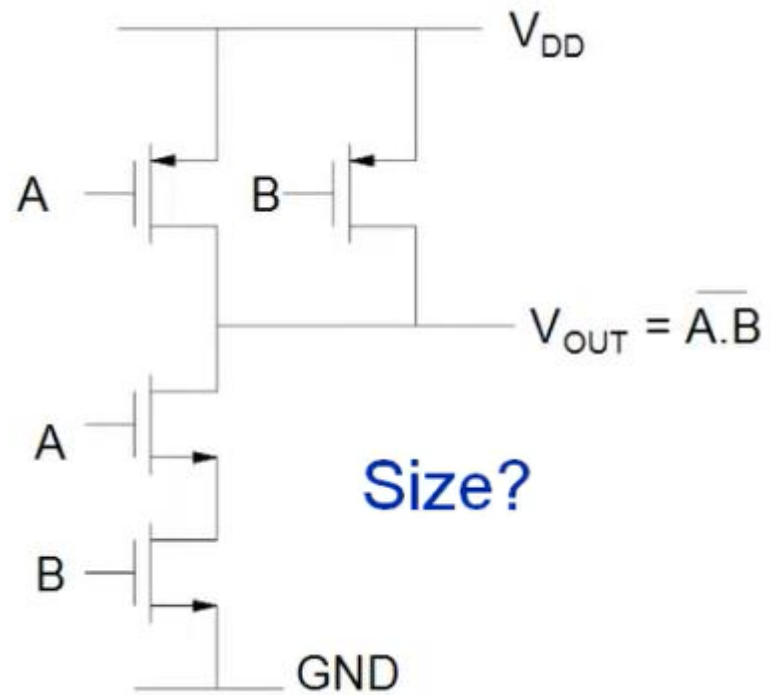

 1. Noise Margins
2. Delay
3. Power
4. Area





1X Inverter

  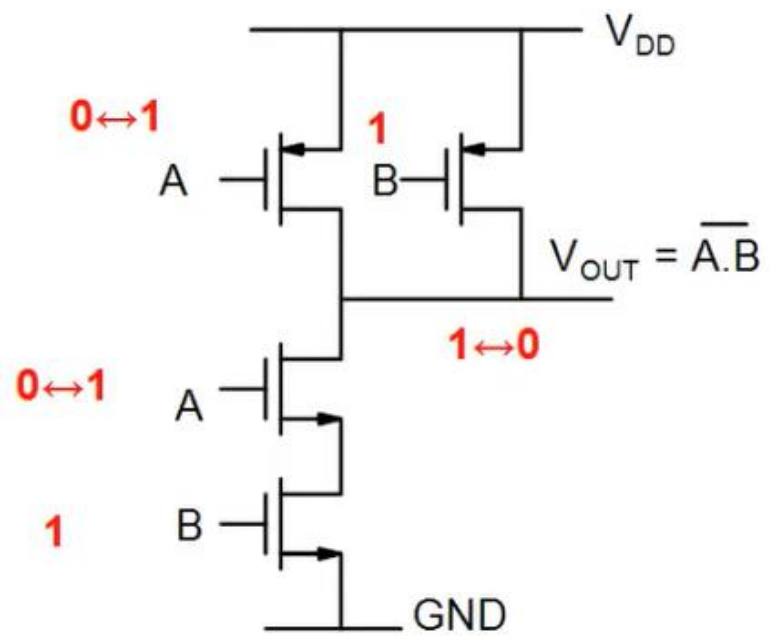




Series Connected Transistors

All transistors are $4\lambda/2\lambda$

 
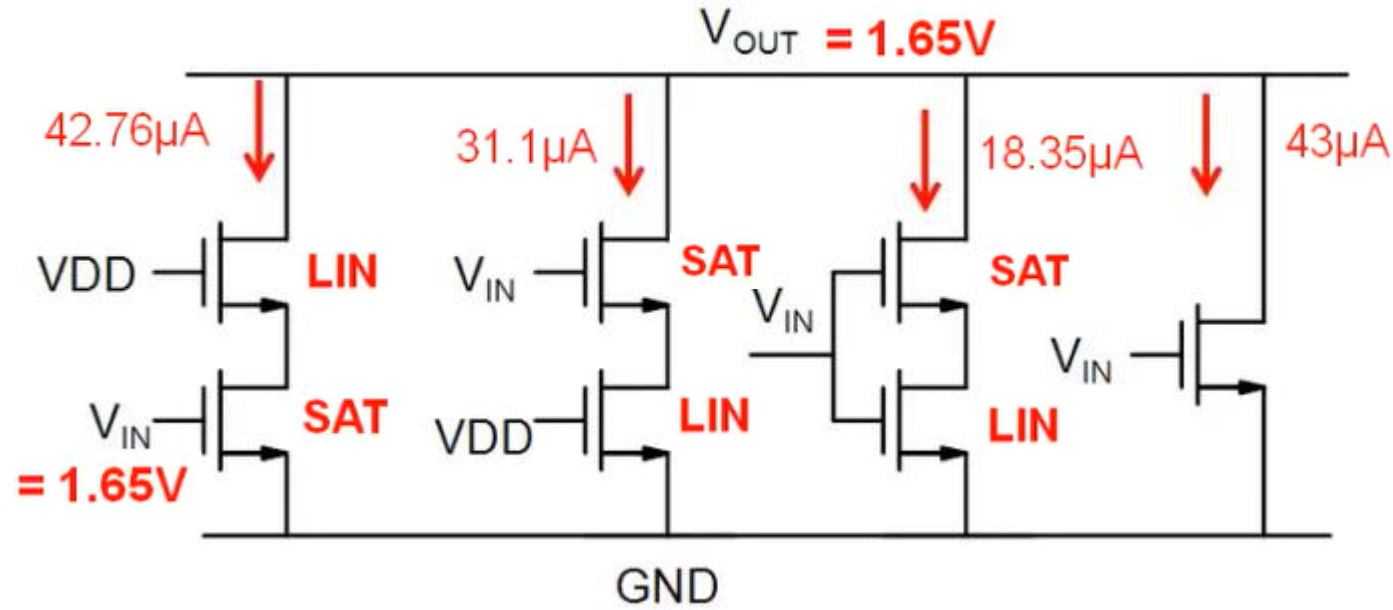


Series Connected Transistors

All transistors are $4\lambda/2\lambda$

 
 
 


2-input CMOS NAND Gate

  


1X Inverter


EC643_DVD_CMOS_NAND2_VTC.cir

   


Case-1

 


Case-2

 

Case-3

 

EC643_DVD_CMOS_NAND2_VTC.cir

 



Case-1 (A): $V_{inv}=1.58V$; $V_{IL}=1.4V$; $V_{IH}=1.72V$


Case-2(B): $V_{inv}=1.53V$; $V_{IL}=1.35V$; $V_{IH}=1.7V$

Case-3 (AB): $V_{inv}=1.78V$; $V_{IL}=1.67V$; $V_{IH}=1.96V$


Inverter: $V_{inv}=1.65V$; $V_{IL}=1.48V$; $V_{IH}=1.814V$

EC643_DVD_CMOS_NAND2_transient_lumped_cap.cir

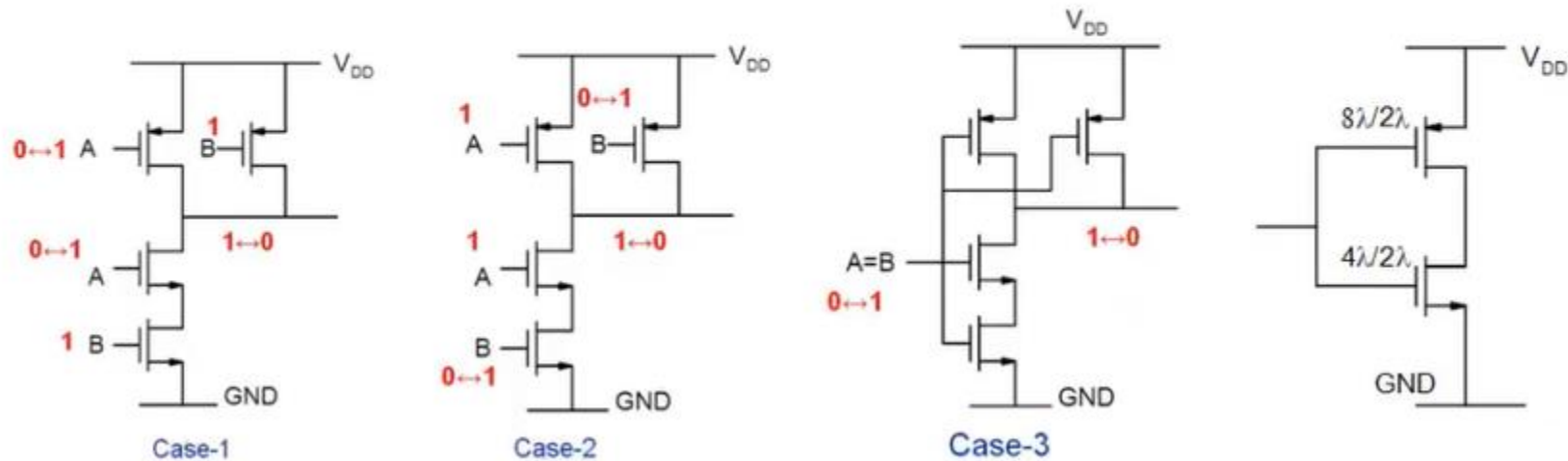 


 

NOR2


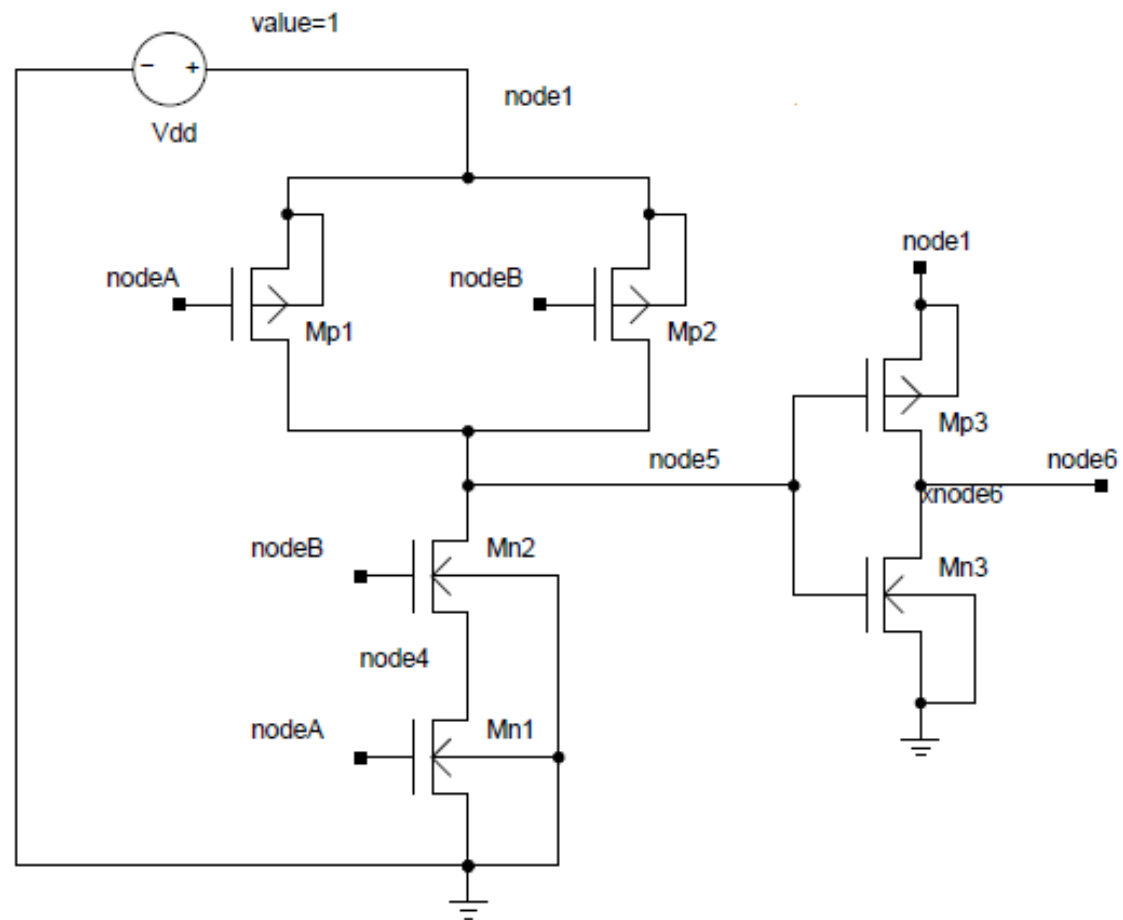


AND2

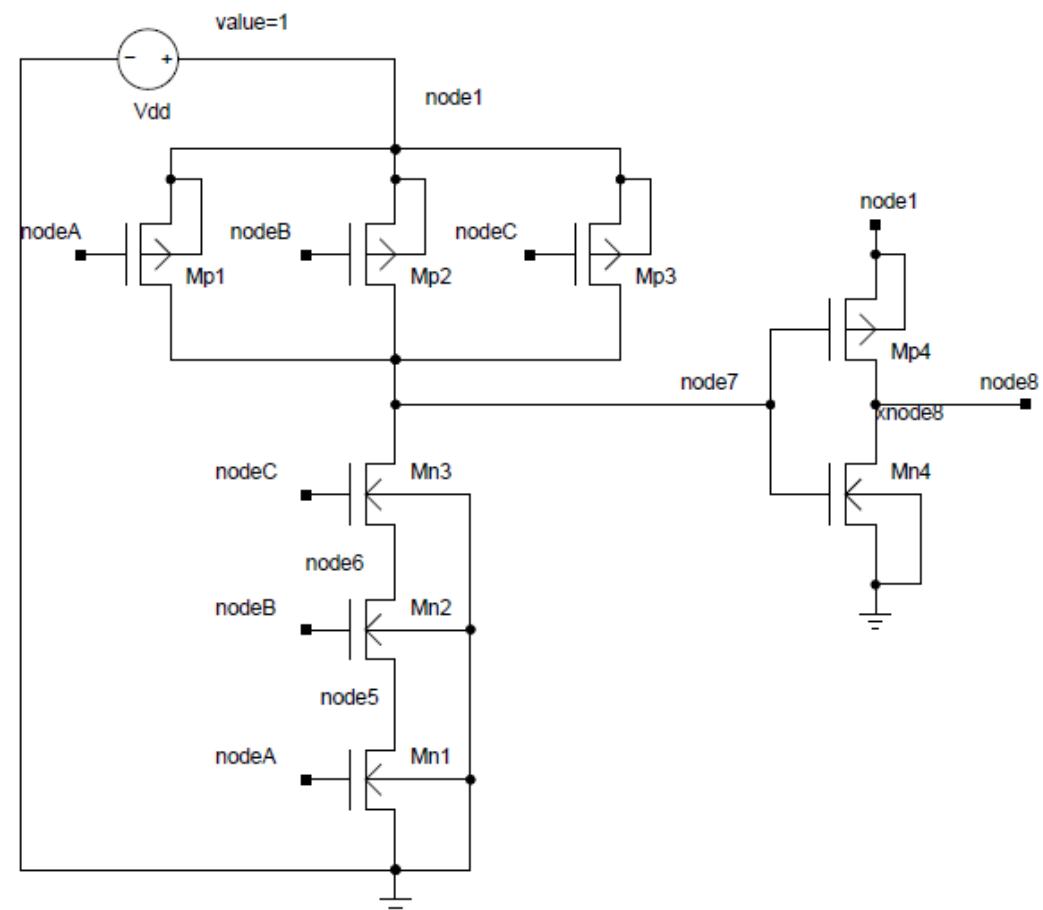

AND3

AB+C

 
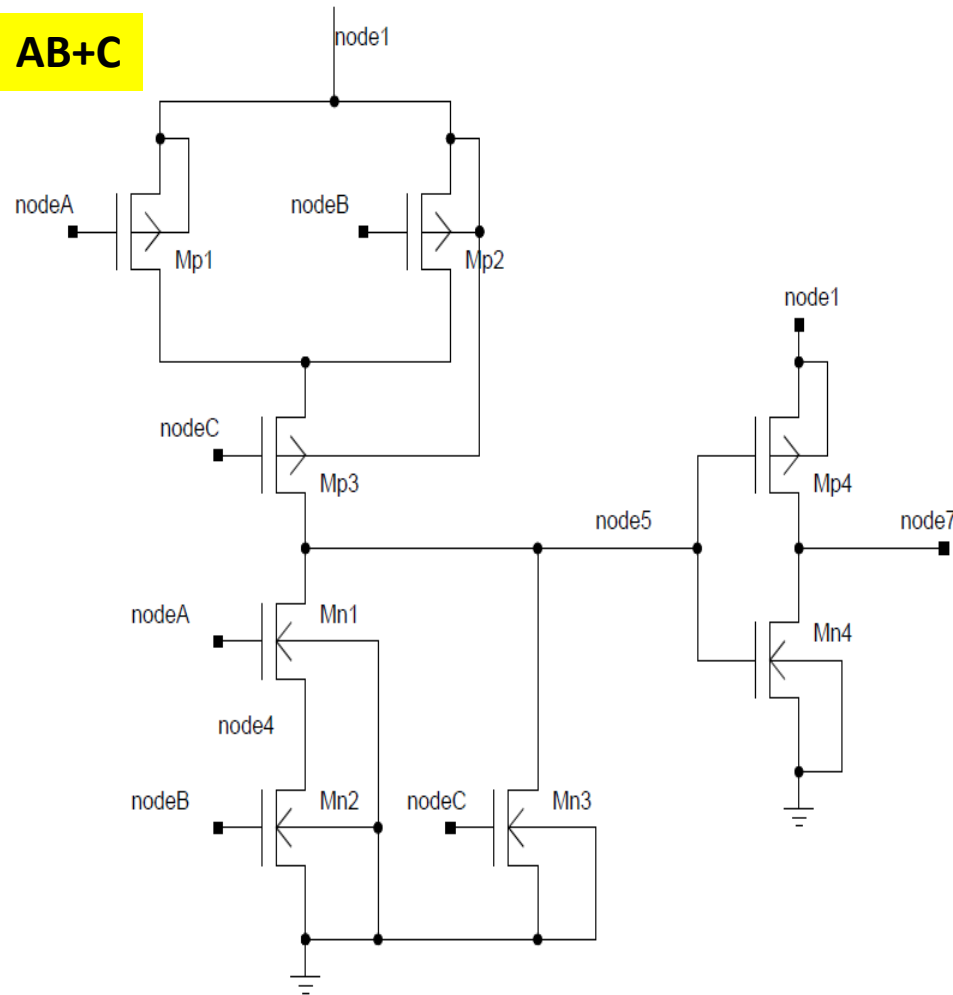


AO12

Design

ABC+DE



OAI21 (Or-And-Invert)

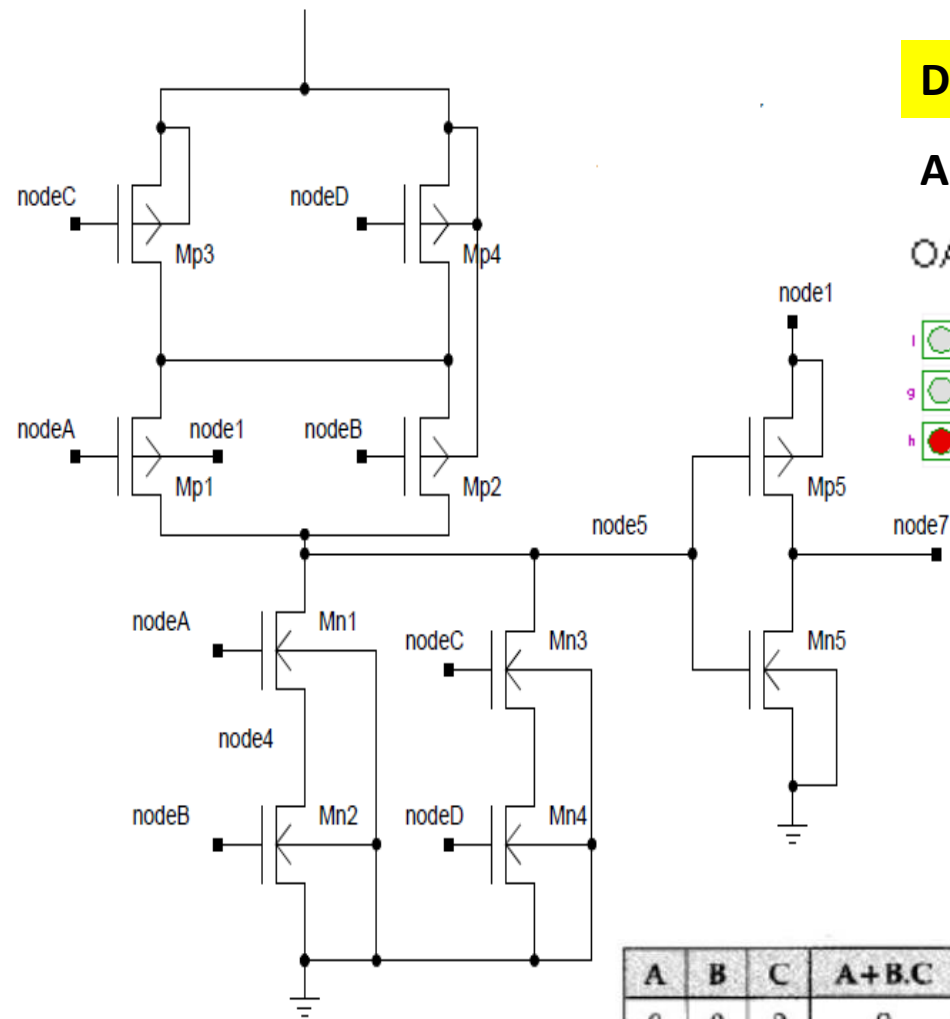 

AO22


A	B	C	A+B.C	A+B	A+C	(A+B).(A+C)
0	0	0	0	0	0	0
0	0	1	0	0	1	0
0	1	0	0	1	0	0
0	1	1	1	1	1	1
1	0	0	1	1	1	1
1	0	1	1	1	1	1
1	1	0	1	1	1	1
1	1	1	1	1	1	1

A031

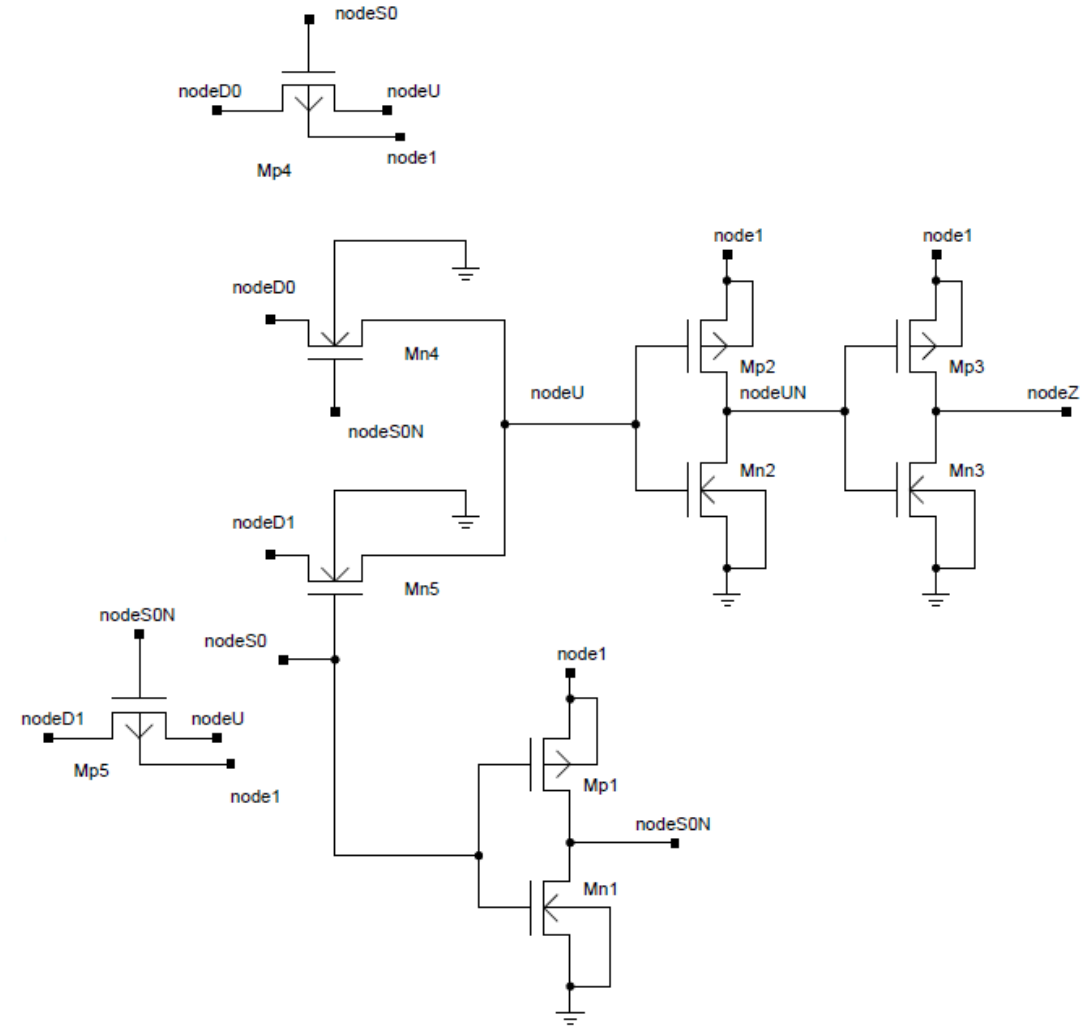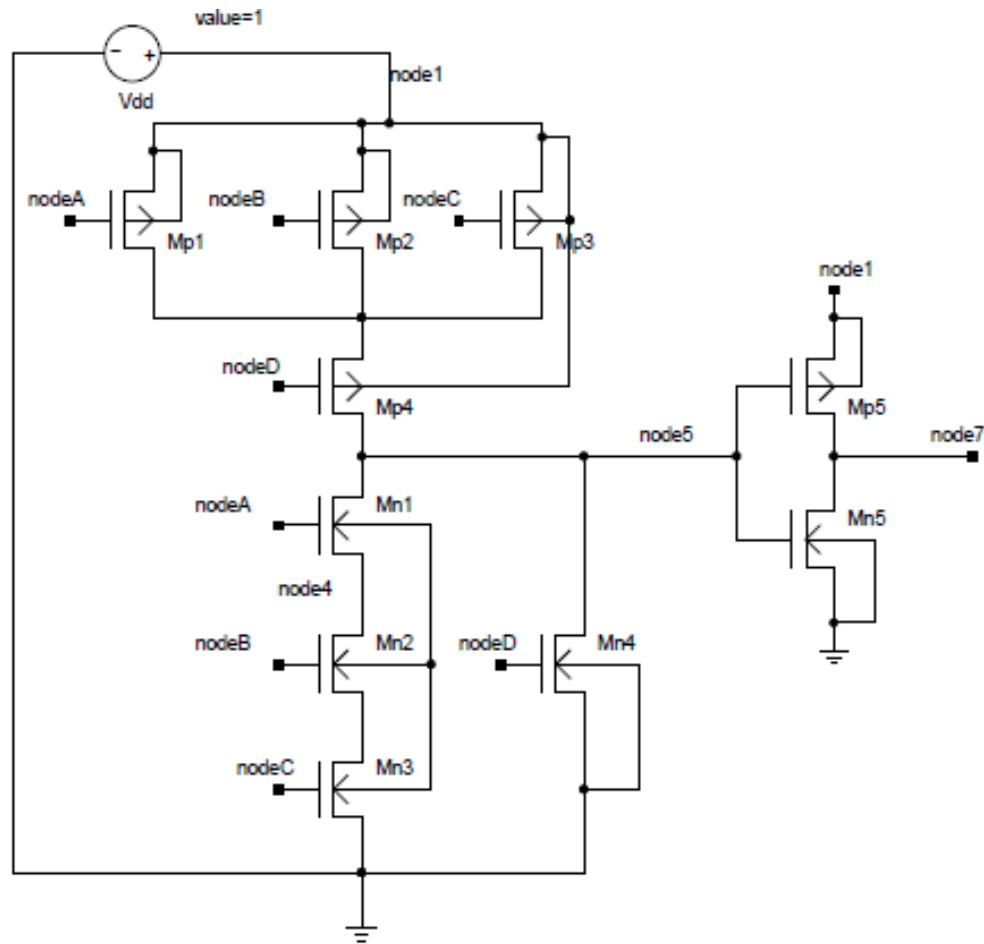

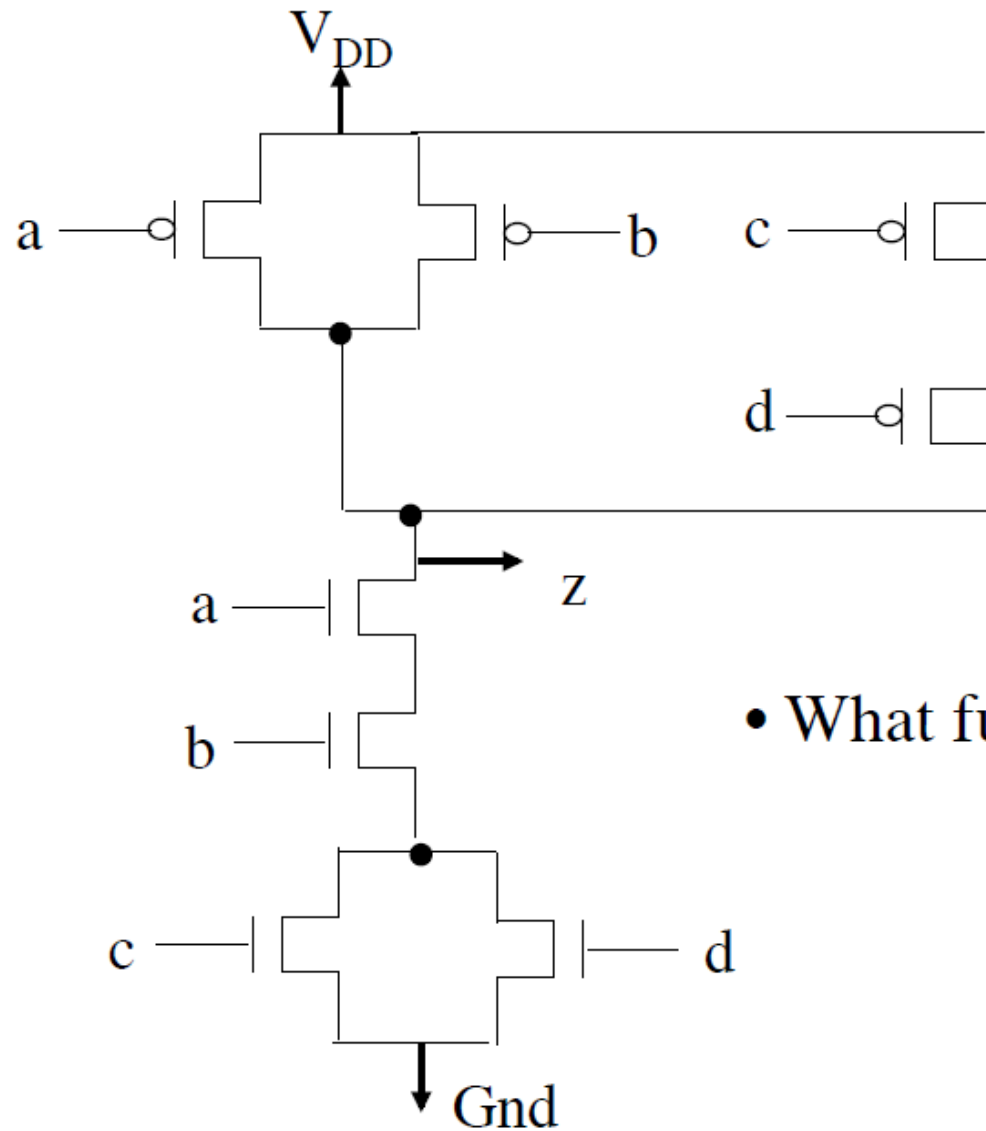
2:1 MUX

How to design? $Y = \overline{(A + B + C)} \cdot D$



- What function is implemented by this circuit?



How to implement
 $F = ab + bc + ca$?



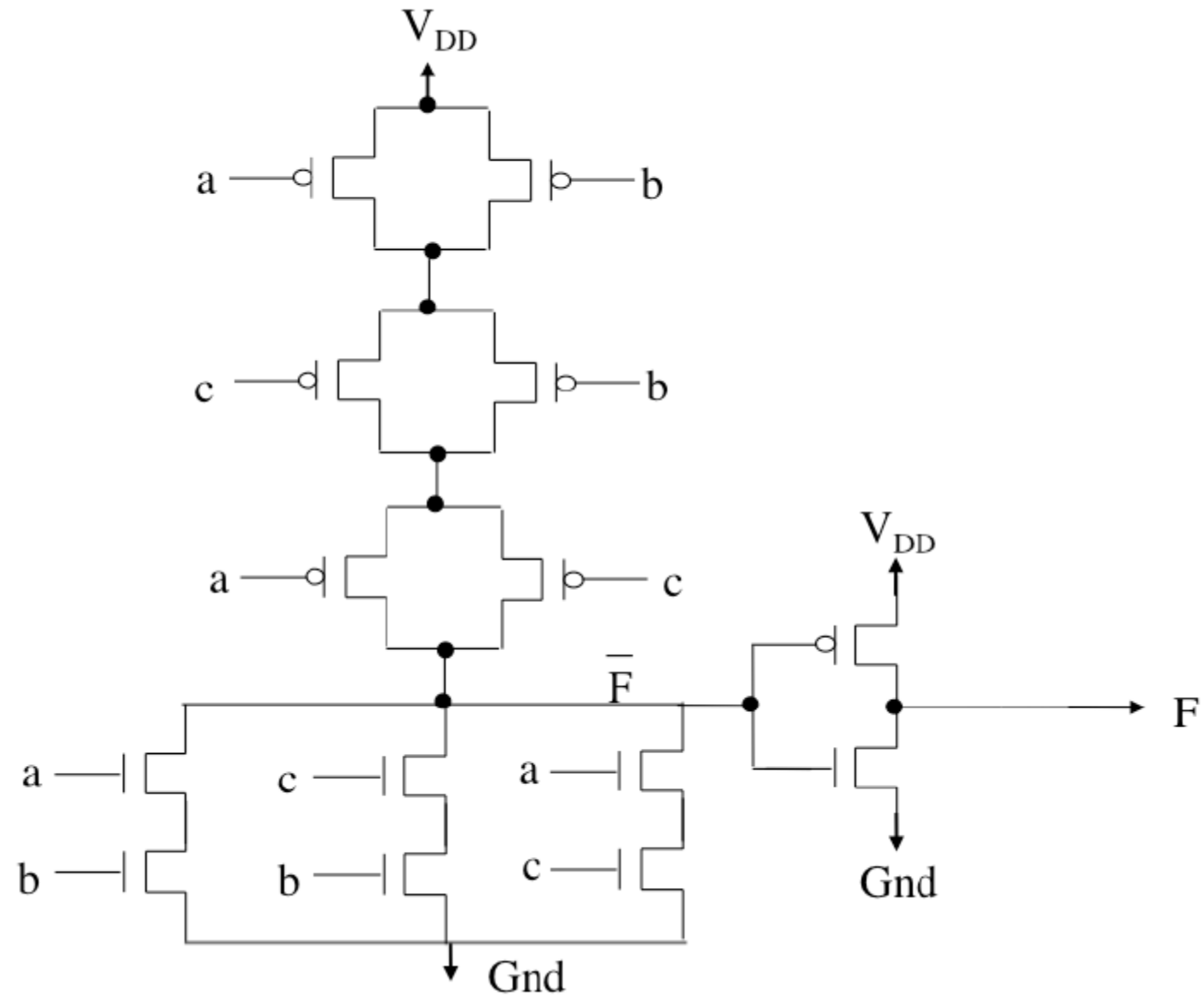


Besides the AOI and OAI gates for complemented two-level normal forms, we can design compound gates for multilevel expressions as well. For example, Boolean expression


$$Y = \overline{(A + BC) \cdot D}$$

has a pull-down network consisting of a series composition of D and a parallel composition of A and a series composition of B and C .

  

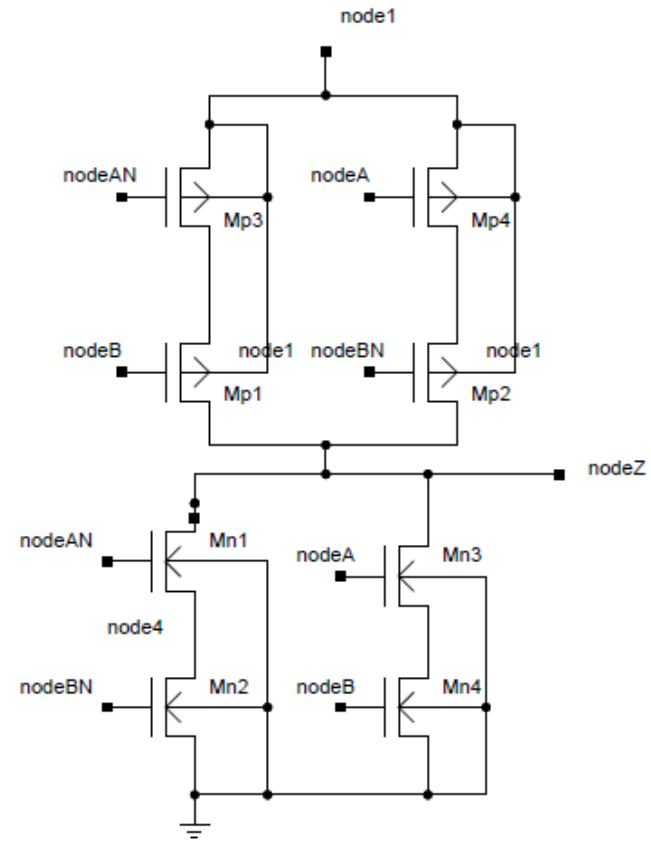  

XOR2

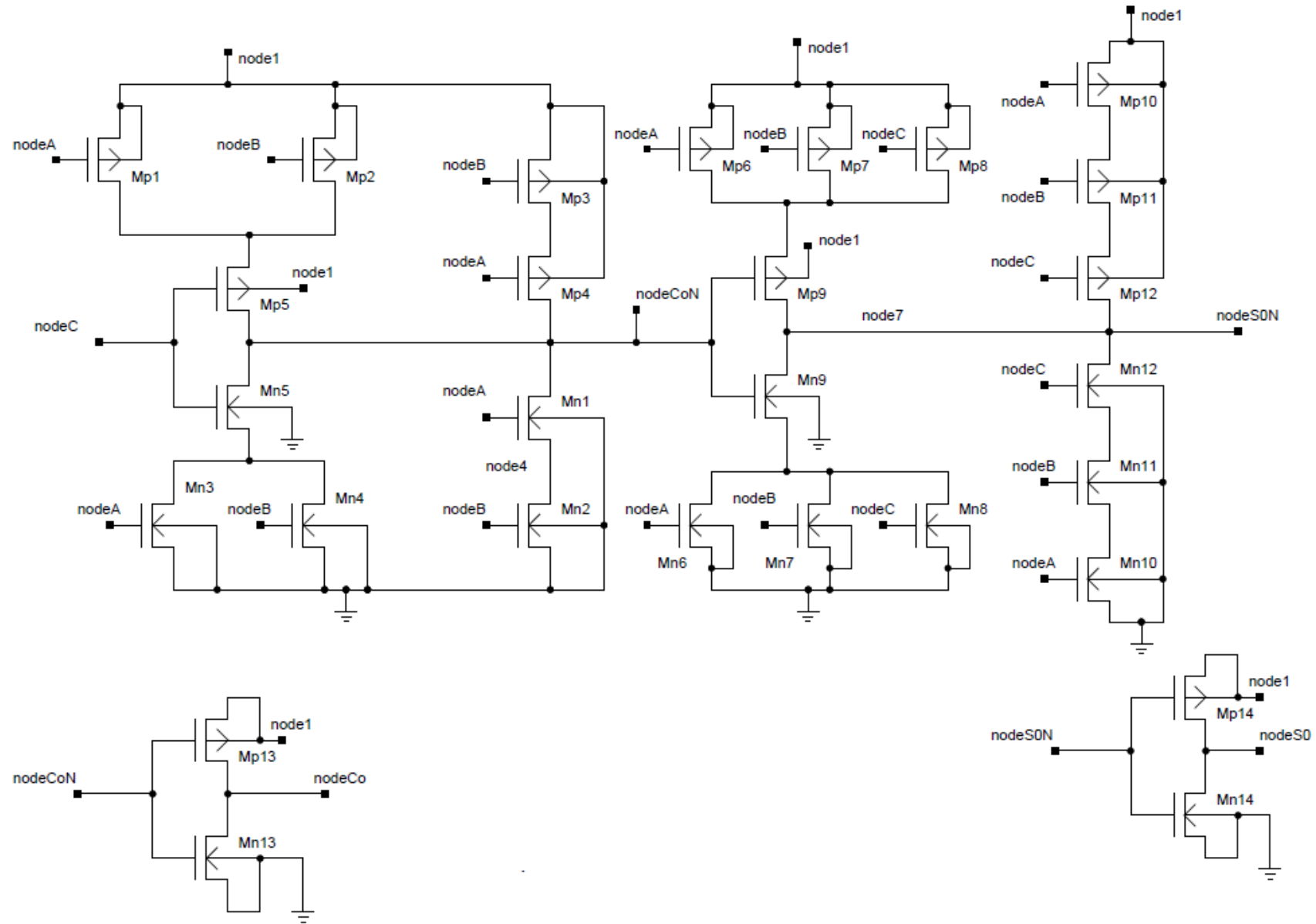

Full Adder

