

$$V_{out} = V_{in}$$




Transistor in saturation

$$I_{DS} = \left( KP_N \times \frac{W}{L} \right) \times \frac{(V_{out} - V_{THN})^2}{2} = \frac{V_{DD} - V_{out}}{R_D}$$

For  $R_D = 72k$ ,  $V_{out} = V_{in} = V_{inv} = 1.5V$


Shift characteristics to right to improve  $NM_L$

1. Decrease  $R_D$
2. Decrease  $W/L$

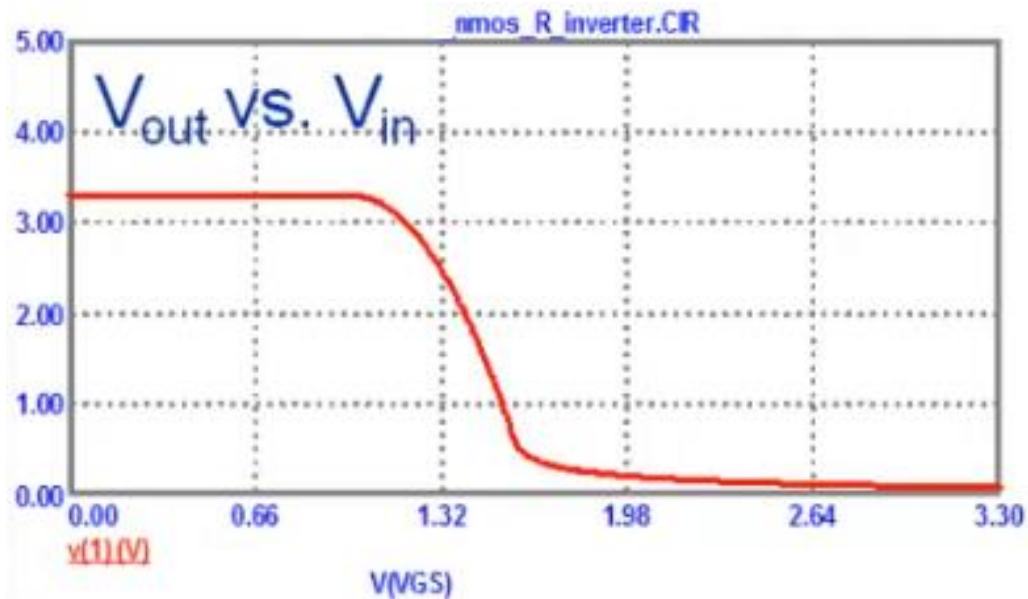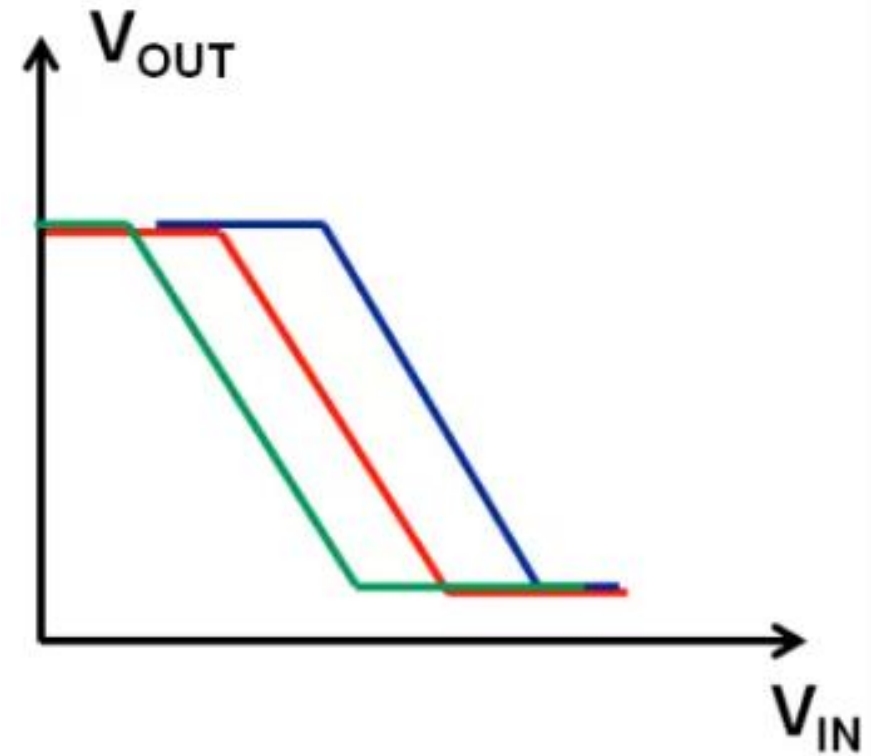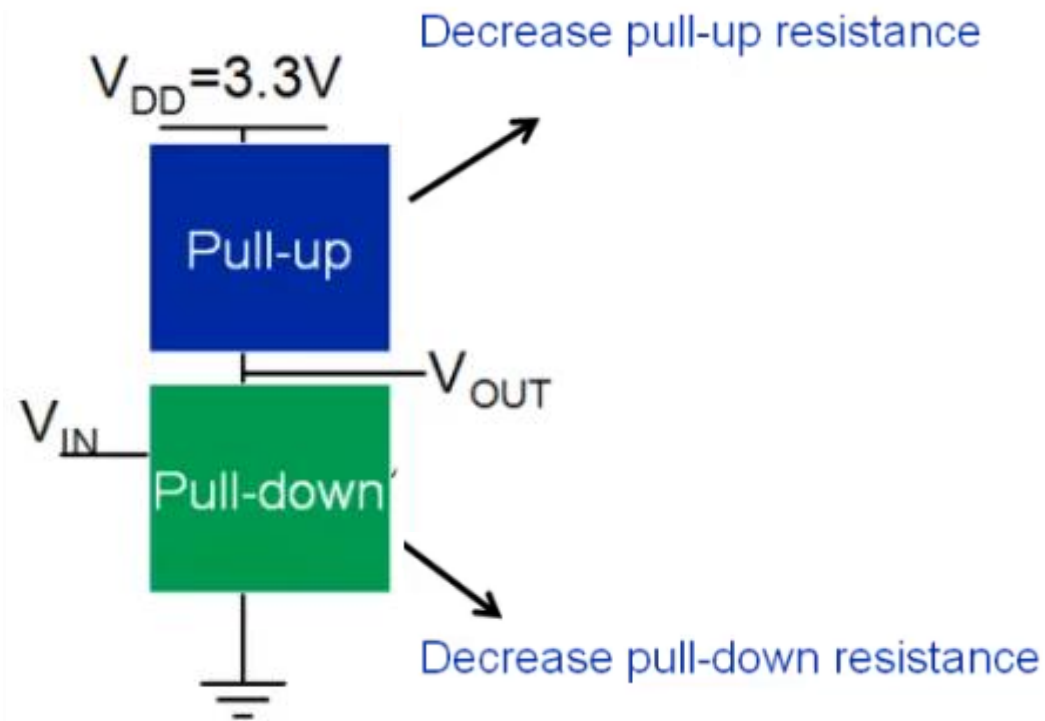


Shift characteristics to right to improve  $NM_L$

1. Decrease  $R_D$
2. Decrease  $W/L$

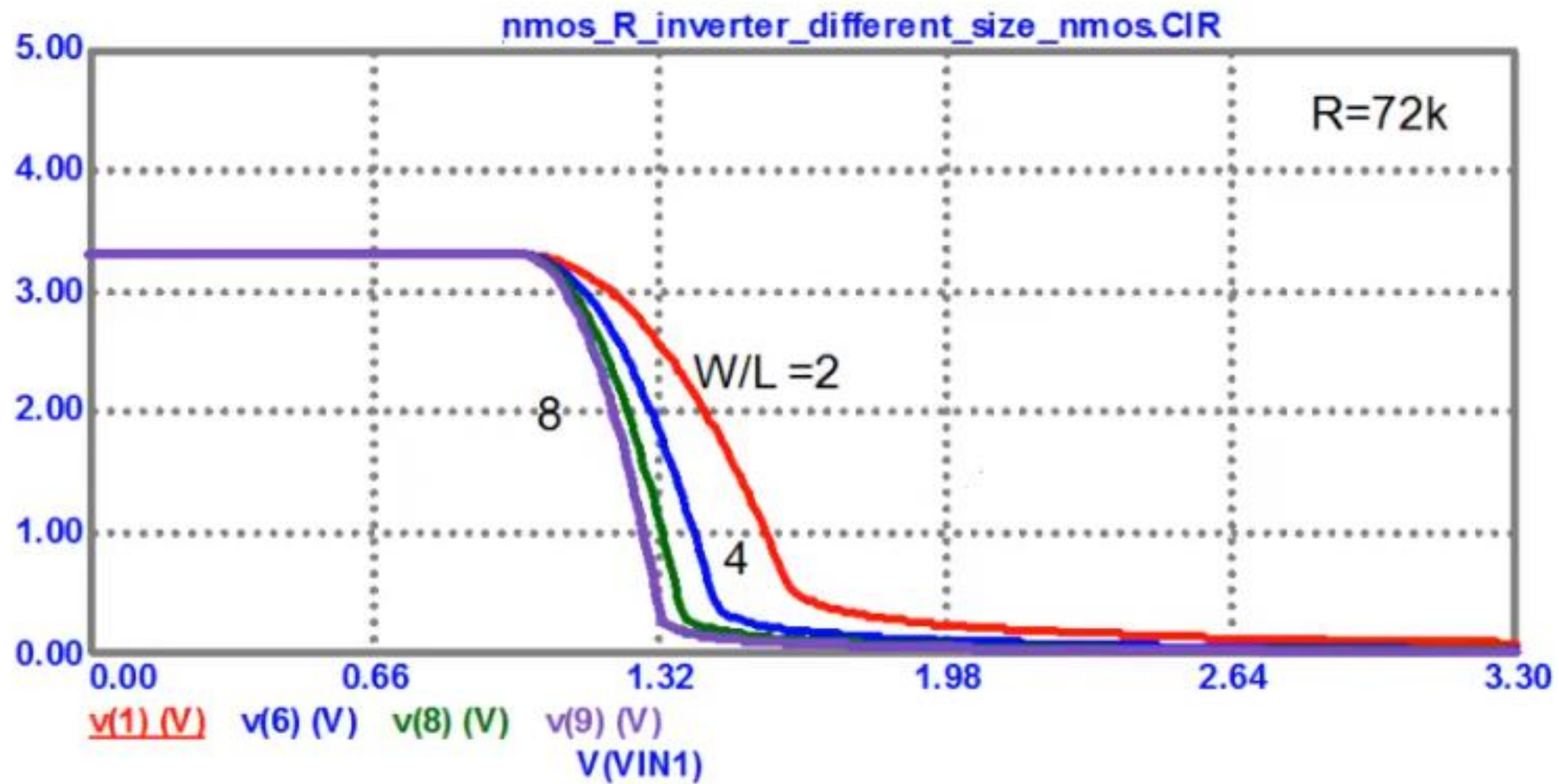

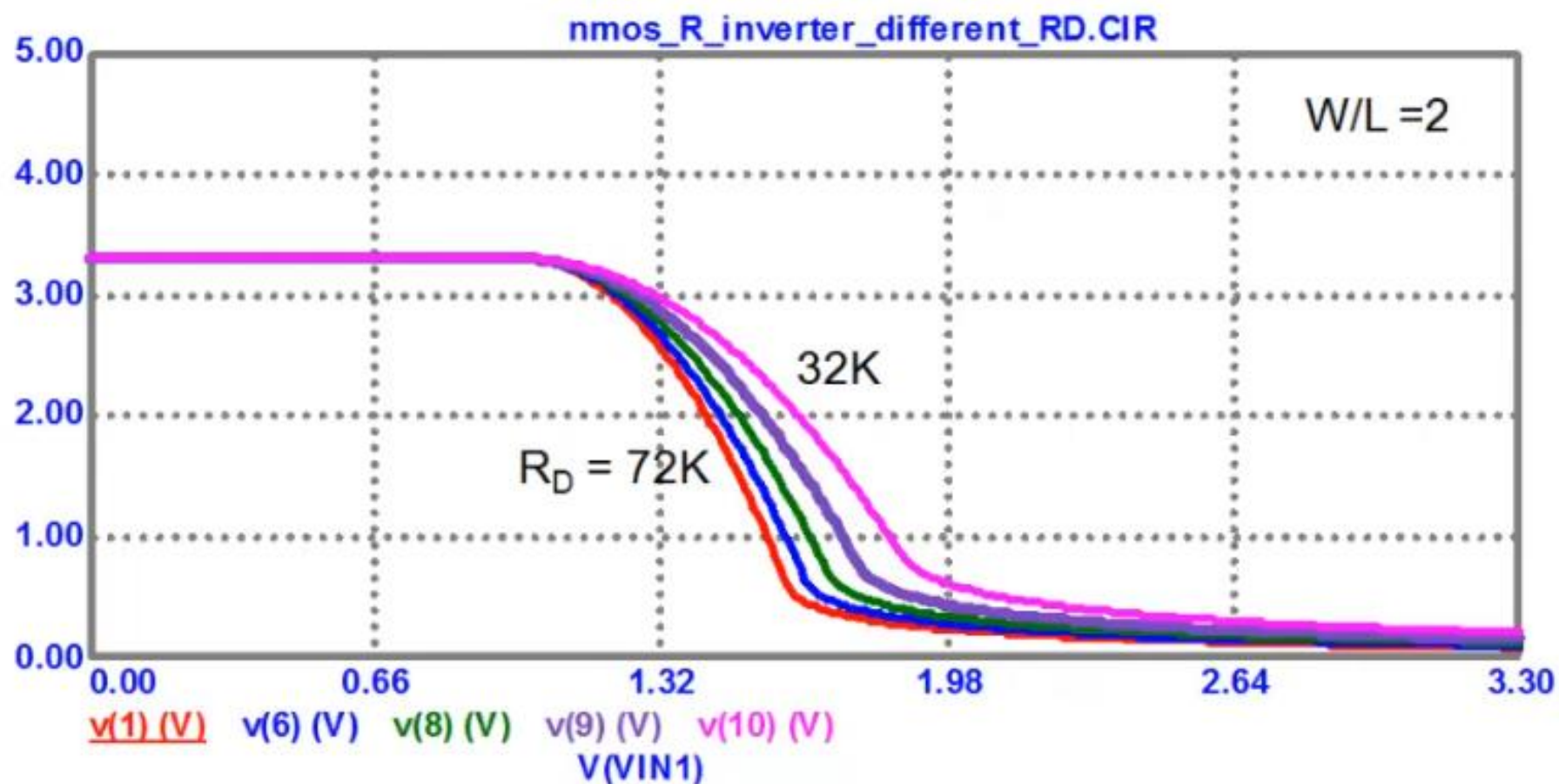Decreasing the pull down resistor shifts characteristics left



$$R_D = 72k \Rightarrow V_{OL} = 0.1V; V_{OH} = 3.3V$$

$$V_{IL} = 1.07V; V_{IH} = 1.7V$$

$$NM_L \sim 0.97V; NM_H \sim 1.6V$$

$$V_{inv} = 1.5V$$


$$R_D = 32k \Rightarrow V_{OL} = 0.22V; V_{OH} = 3.3V$$

$$V_{IL} = 1.16V; V_{IH} = 2V$$

$$NM_L \sim 0.94V; NM_H \sim 1.3V$$

$$V_{inv} = 1.72V$$



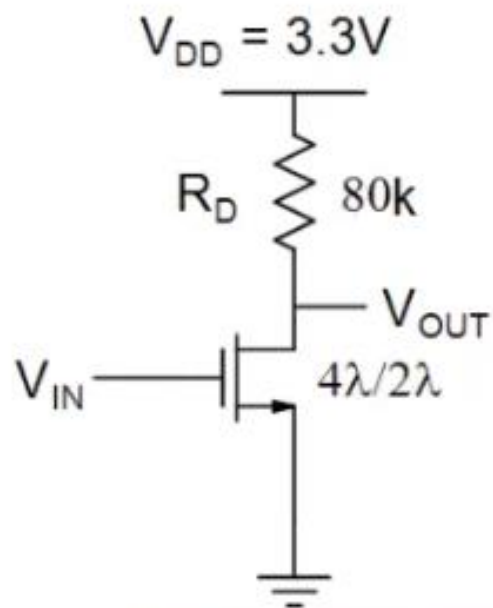


$$NM_L \sim 0.97V; NM_H \sim 1.6V$$

$$R_D = 10k$$

$$W/L = 4\lambda/2\lambda; R_D = 10k \Rightarrow V_{OL} \sim 0.72V$$


$$NM_L = V_{IL} - V_{OL} \sim 0.28V$$

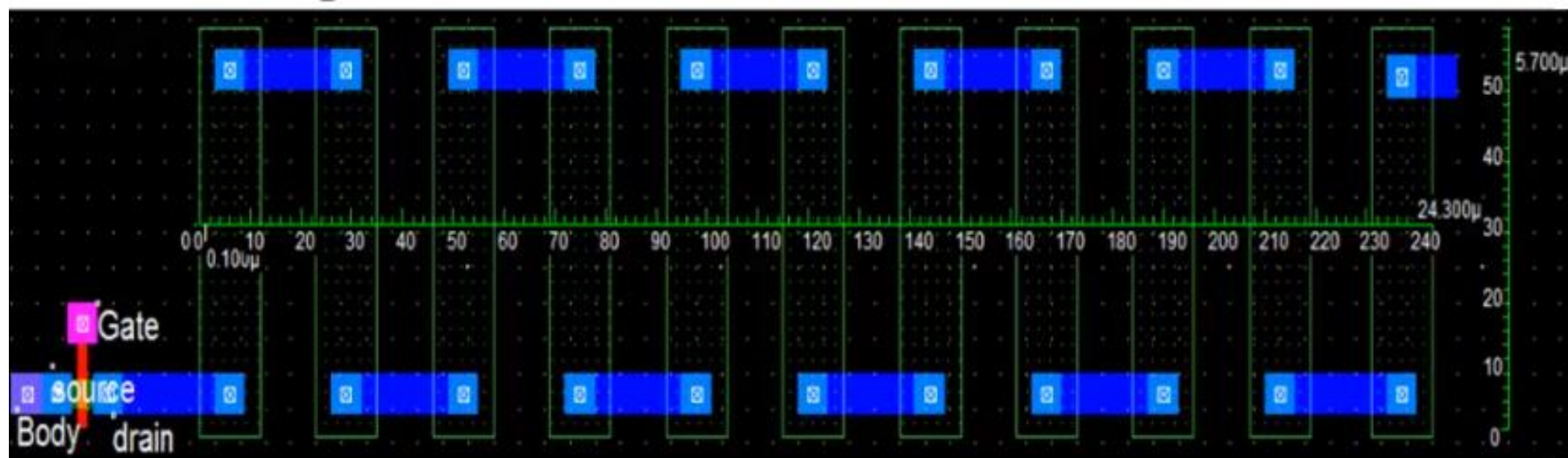1. Area
2. Delay
3. Power
4. Noise Margins




$$\frac{A_{RD}}{A_{tr1}} \sim 35$$



# Propagation Delay

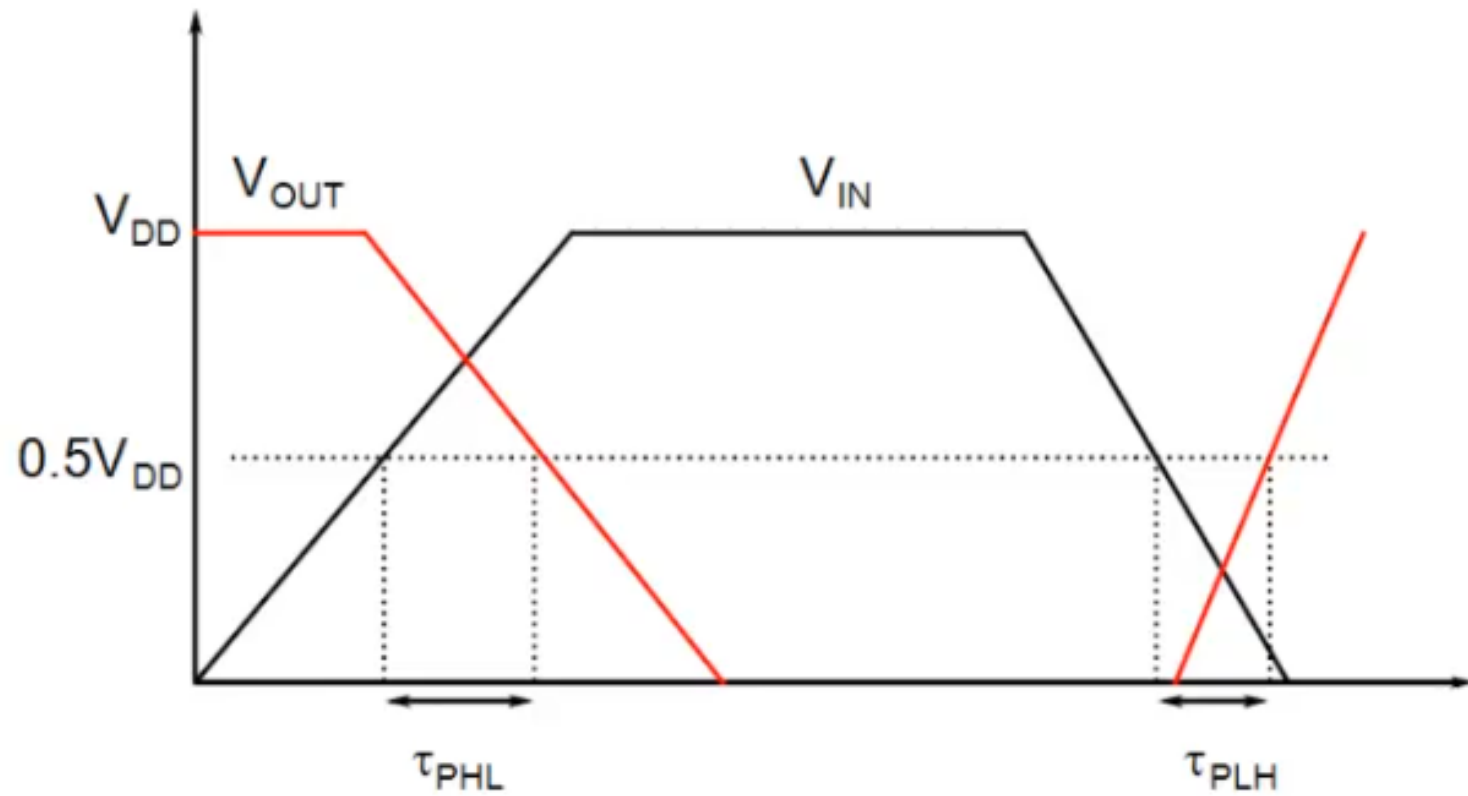




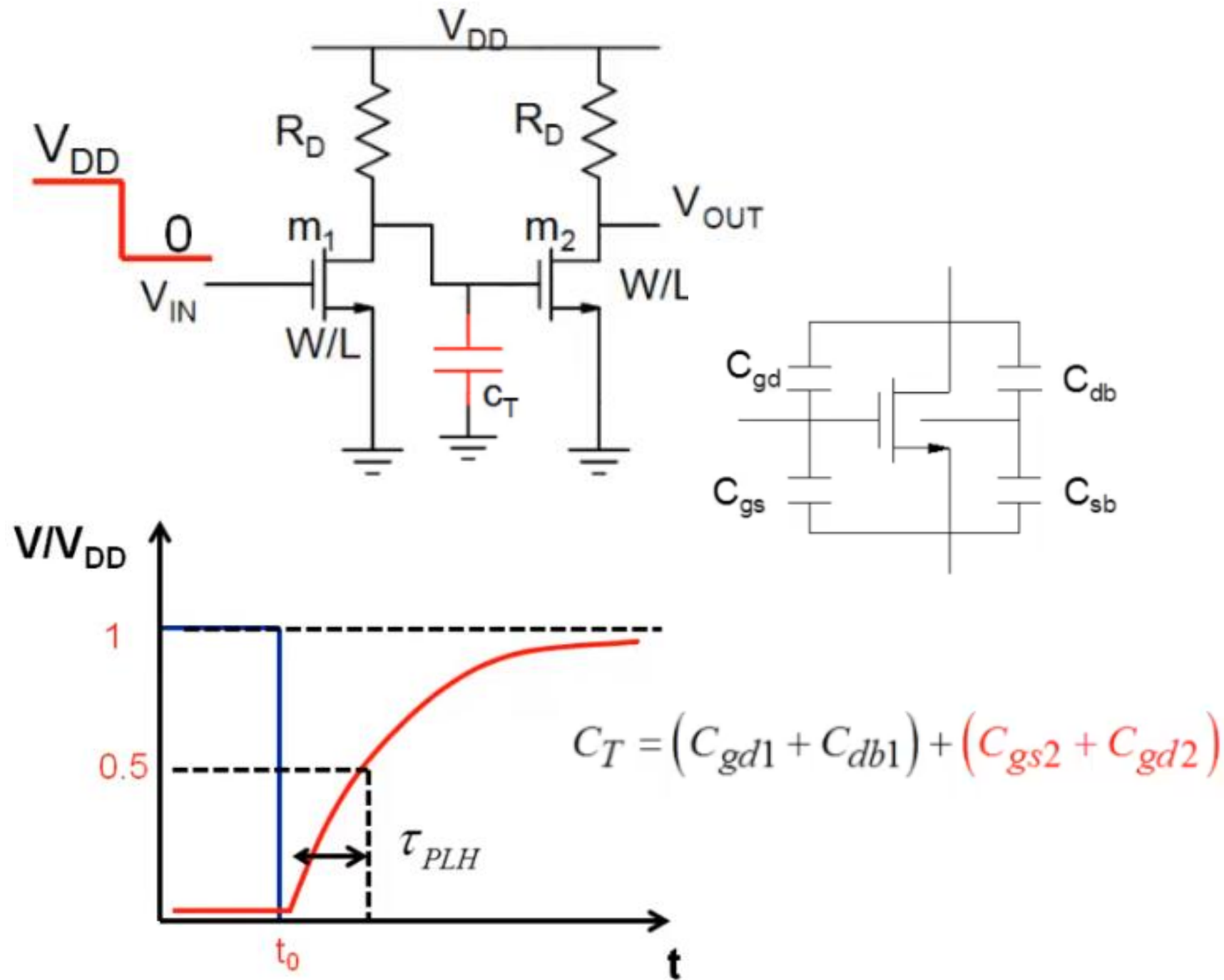
$$\tau_R ; \tau_F ; \tau_{PHL} ; \tau_{PLH}$$



| Parameter                     | NMOS   | PMOS   |
|-------------------------------|--------|--------|
| $V_{THNO}(V)$                 | 0.69   | -0.869 |
| $\lambda$ (for $L = 1\mu m$ ) | 0.015  | 0.065  |
| $\gamma$                      | 0.696  | 0.456  |
| $KP (\mu A/V^2)$              | 100    | 40     |
| $CGSO (pF)$                   | 281    | 252    |
| $CGDO (pF/m)$                 | 281    | 252    |
| $CJ (\mu F/m^2)$              | 467.7  | 932    |
| $PB$                          | 0.9    | 0.92   |
| $MJ$                          | 0.5    | 0.466  |
| $CJSW (pF/m)$                 | 616.95 | 181    |
| $MJSW$                        | 0.235  | 0.5    |

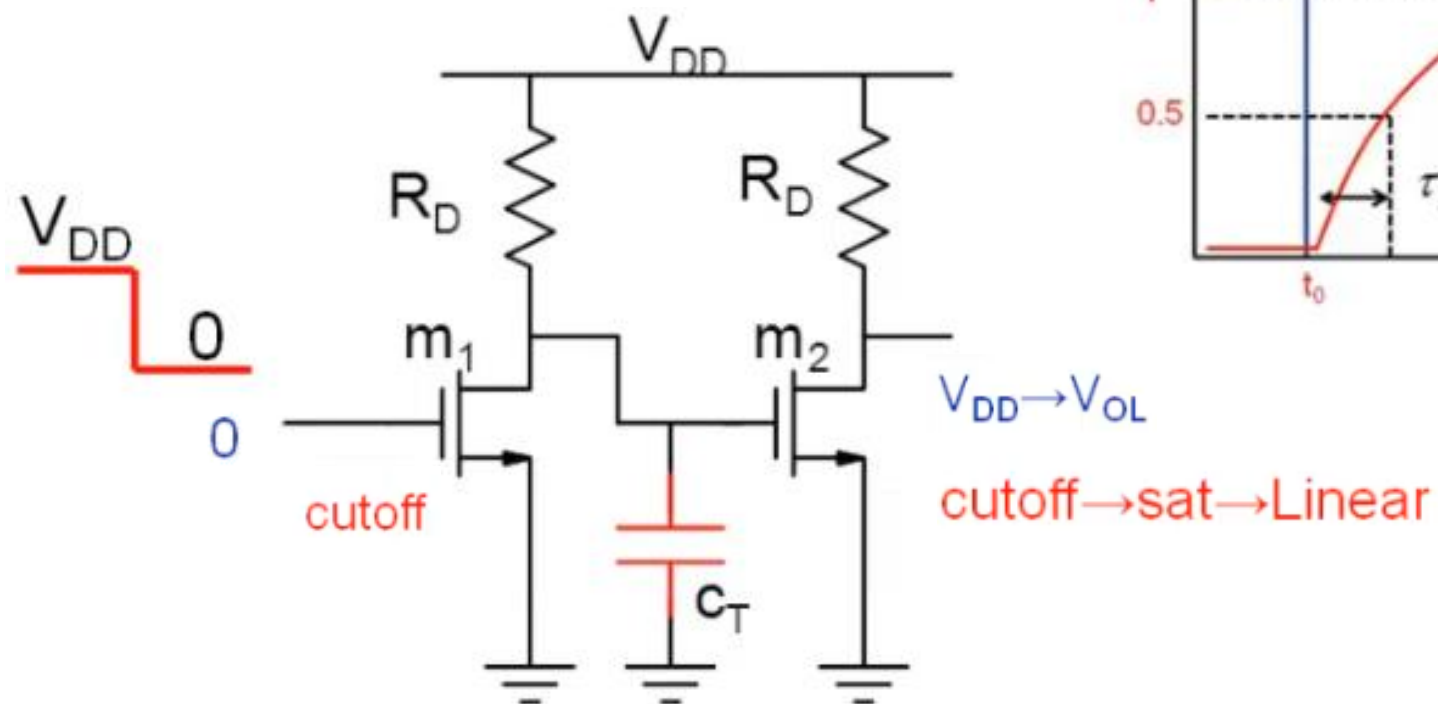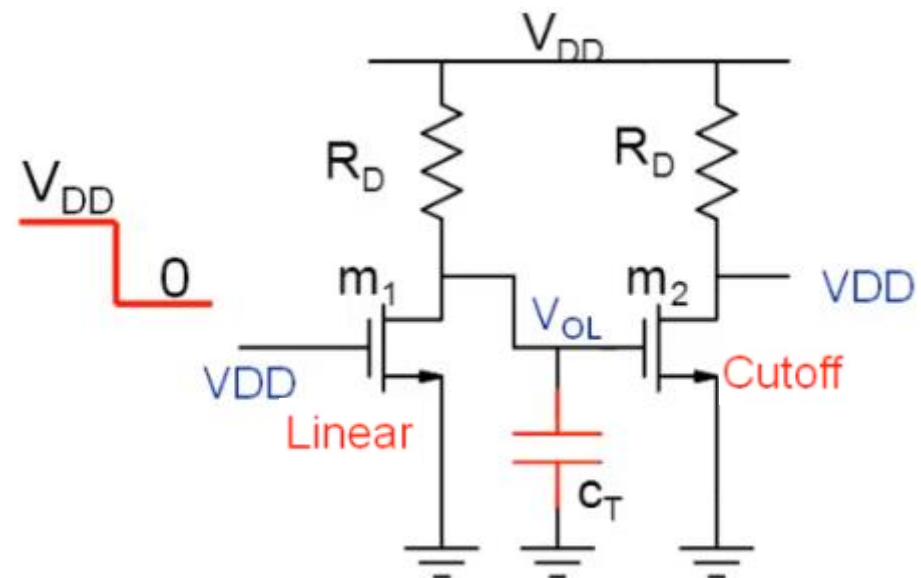



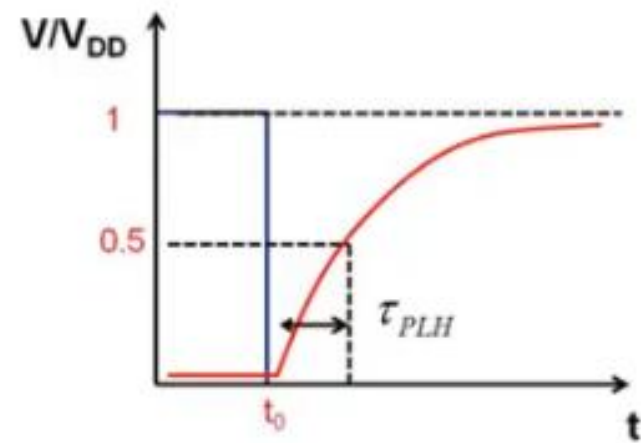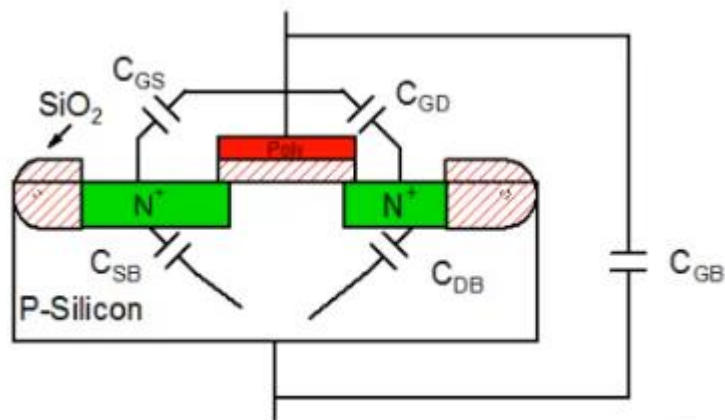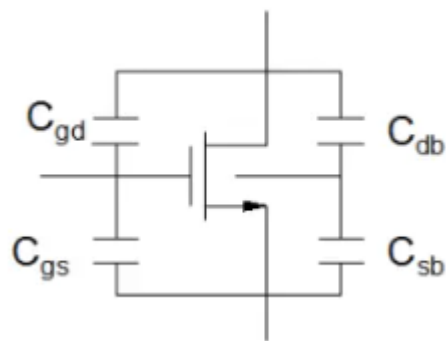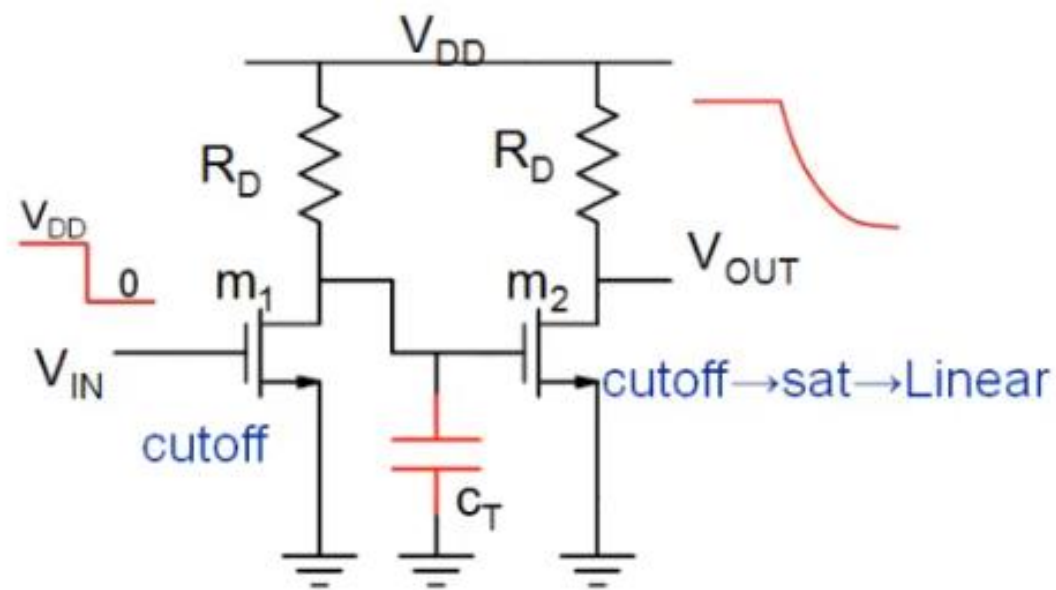


$$C_T = (C_{gd1} + C_{db1}) + (C_{gs2} + C_{gd2})$$

$$C_{gd1} = C_{GDO} \cdot W_1 \quad C_{gd2} = C_{GDO} \cdot W_2$$

$$C_{db1} = \frac{C_{jsw} \cdot P_D}{\left(1 + \frac{V_{DB}}{P_{BSW}}\right)^{M_{jsw}}} + \frac{C_j \cdot A_D}{\left(1 + \frac{V_{DB}}{P_B}\right)^{M_j}}$$

$V_{DB} = 0 \rightarrow 0.5V_{DD}$
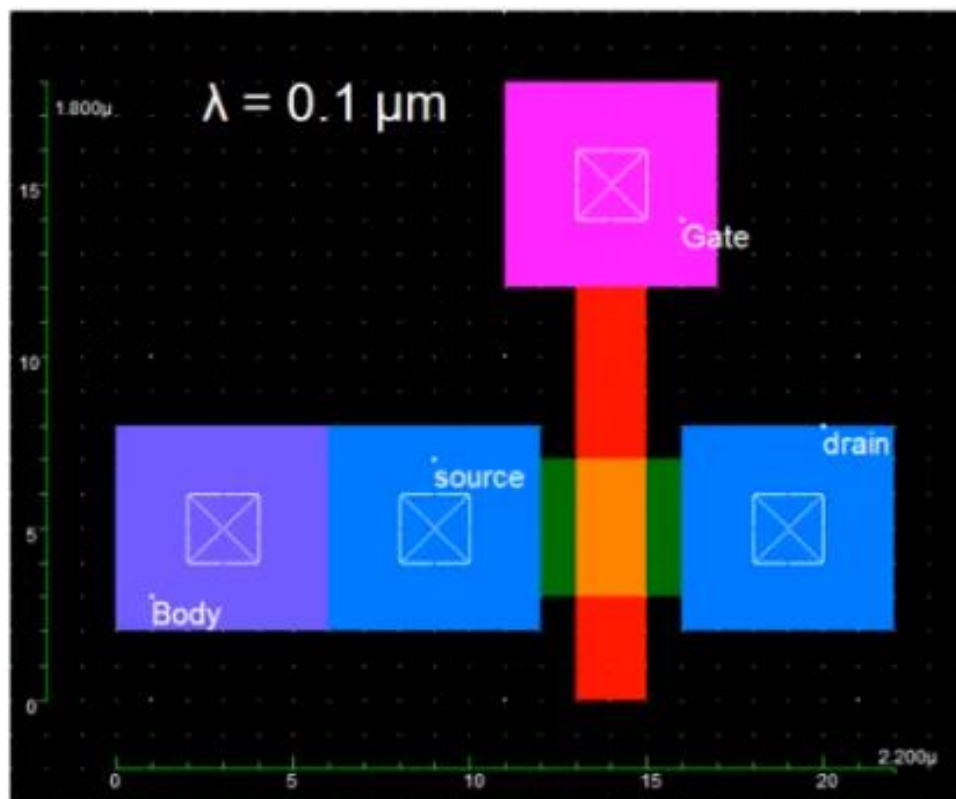
$$C_{gs1} \cong (C_{gso} \cdot W) \rightarrow \frac{2}{3} C_{ox'} \cdot W \cdot L + C_{gso} \cdot W$$




$$A_D = 4 \times 1 + 6 \times 6 = 40;$$

$$P_D = 2 \times (1 + 1 + 6) + 6 = 22$$

$$V_{DB} = 0$$

$$C_{db1} = \frac{C_{jsw} \cdot P_D}{\left(1 + \frac{V_{DB}}{P_{BSW}}\right)^{M_{jsw}}} + \frac{C_j \cdot A_D}{\left(1 + \frac{V_{DB}}{P_B}\right)^{M_j}} = 5.7 \text{ fF}$$

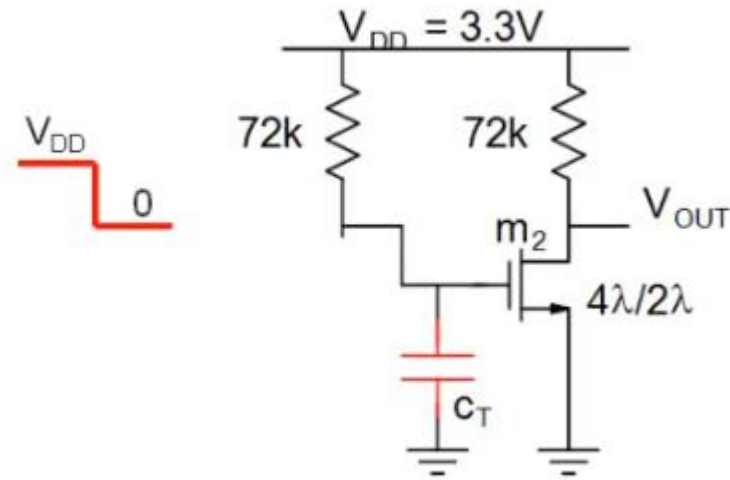$\nwarrow$   $\sim 4 \text{ fF}$ 
 $\swarrow$   $1.7 \text{ fF}$





$$C_T = (C_{gd1} + C_{db1}) + (C_{gs2} + C_{gd2})$$

$$C_{To} = 8.5 fF$$

$$\begin{aligned} \tau_{PLH} &\cong 0.693 \times R_D \times \tilde{C}_T \\ &= 424 ps \end{aligned}$$
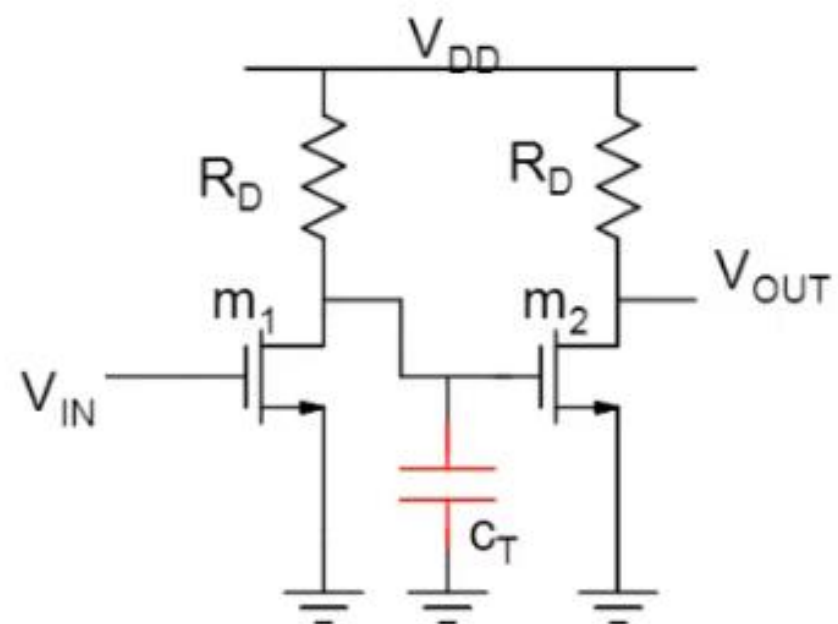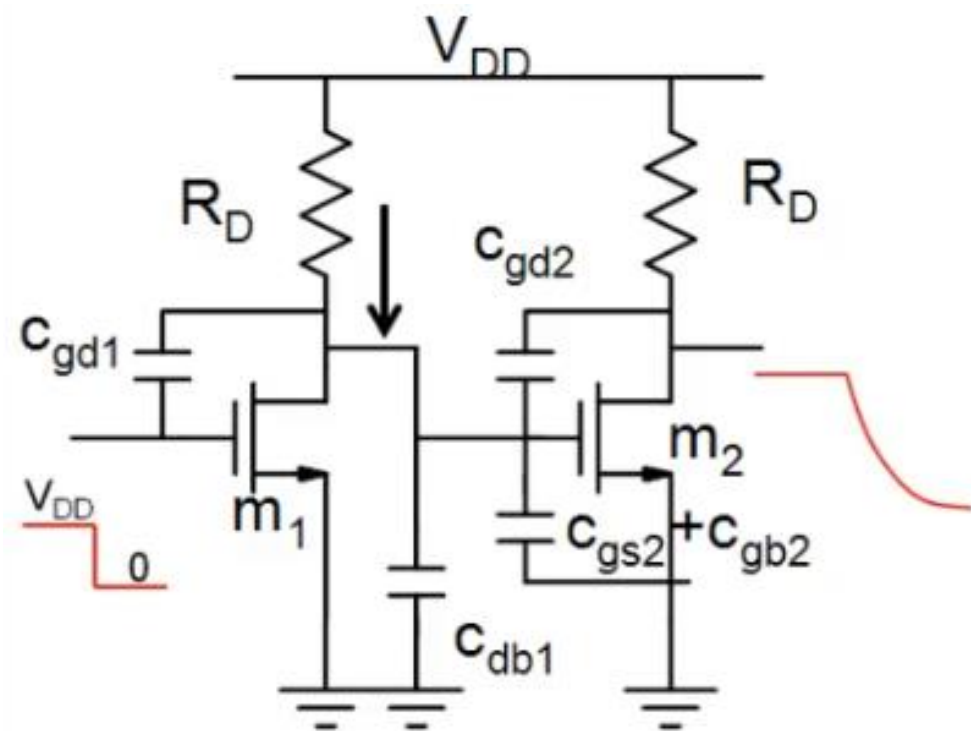
$$\tau_{PLH} \cong 137 ps \text{ if } C_{db} \text{ is not considered}$$



M1 : linear  $\rightarrow$  cutoff



M2: cutoff  $\rightarrow$  sat  $\rightarrow$  Linear

$$C_T = (C_{gd1} + C_{db1}) + (C_{gs2} + C_{gd2} + C_{gb2})$$

$$I = \sum \frac{dQ_j}{dt}$$

$$I = C_{gd1} \times \frac{d(V_{D1} - V_{G1})}{dt} + C_{gd2} \times \frac{d(V_{D1} - V_{D2})}{dt} + C_{db1} \times \frac{dV_{D1}}{dt} + (C_{gs2} + C_{gb2}) \times \frac{dV_{D1}}{dt}$$
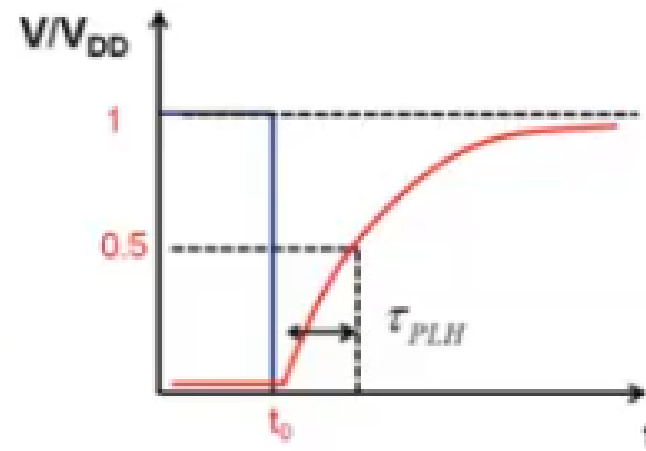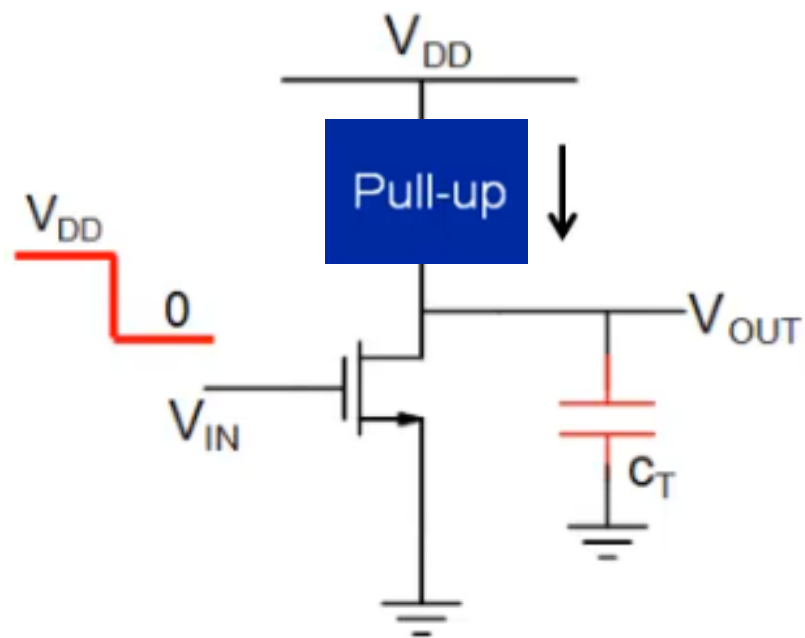
$$I = \left( C_{gd1} \times \left( 1 - \frac{dV_{G1}}{dV_{D1}} \right) + C_{gd2} \times \left( 1 - \frac{dV_{D2}}{dV_{D1}} \right) + C_{db1} + C_{gs2} + C_{gb2} \right) \times \frac{dV_{D1}}{dt}$$




$$I_{pu} = C_T \times \frac{dV_{out}}{dt}$$


$$\tau_{plh} = \int_0^{0.5V_{DD}} \frac{C_T}{I_{pu}} \times dV_{out}$$
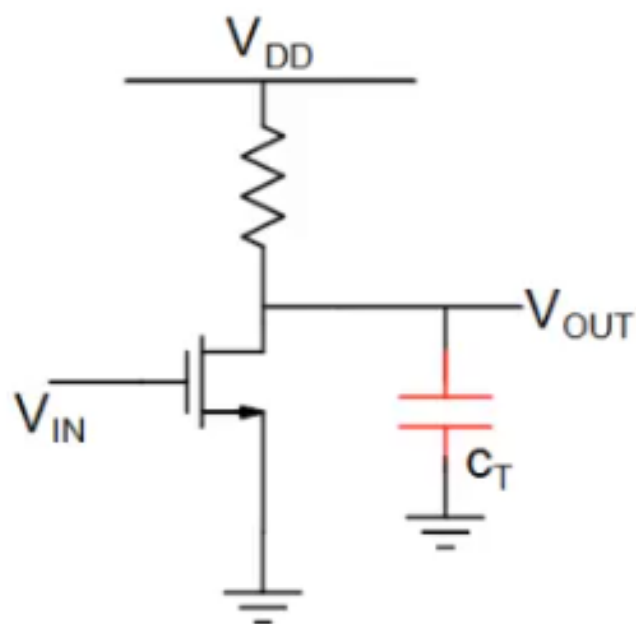
$$\tau_{plh} \cong 0.5 \times \frac{\tilde{C}_T V_{DD}}{\tilde{I}_{pu}}$$





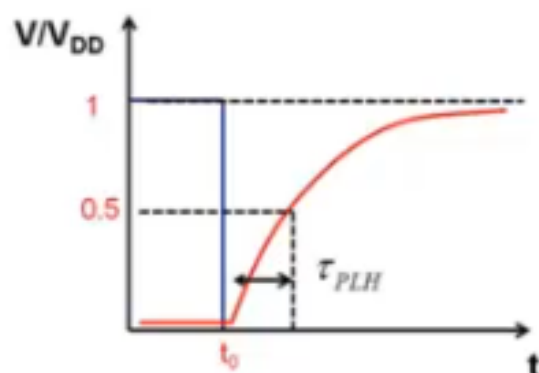
$$\tau_{plh} \cong 0.5 \times \frac{\tilde{C}_T V_{DD}}{\tilde{I}_{pu}}$$



$$I_{pu} = \frac{V_{DD}}{R_D} \rightarrow \frac{0.5V_{DD}}{R_D}$$

$$\tilde{I}_{pu} \cong 0.75 \frac{V_{DD}}{R_D}$$
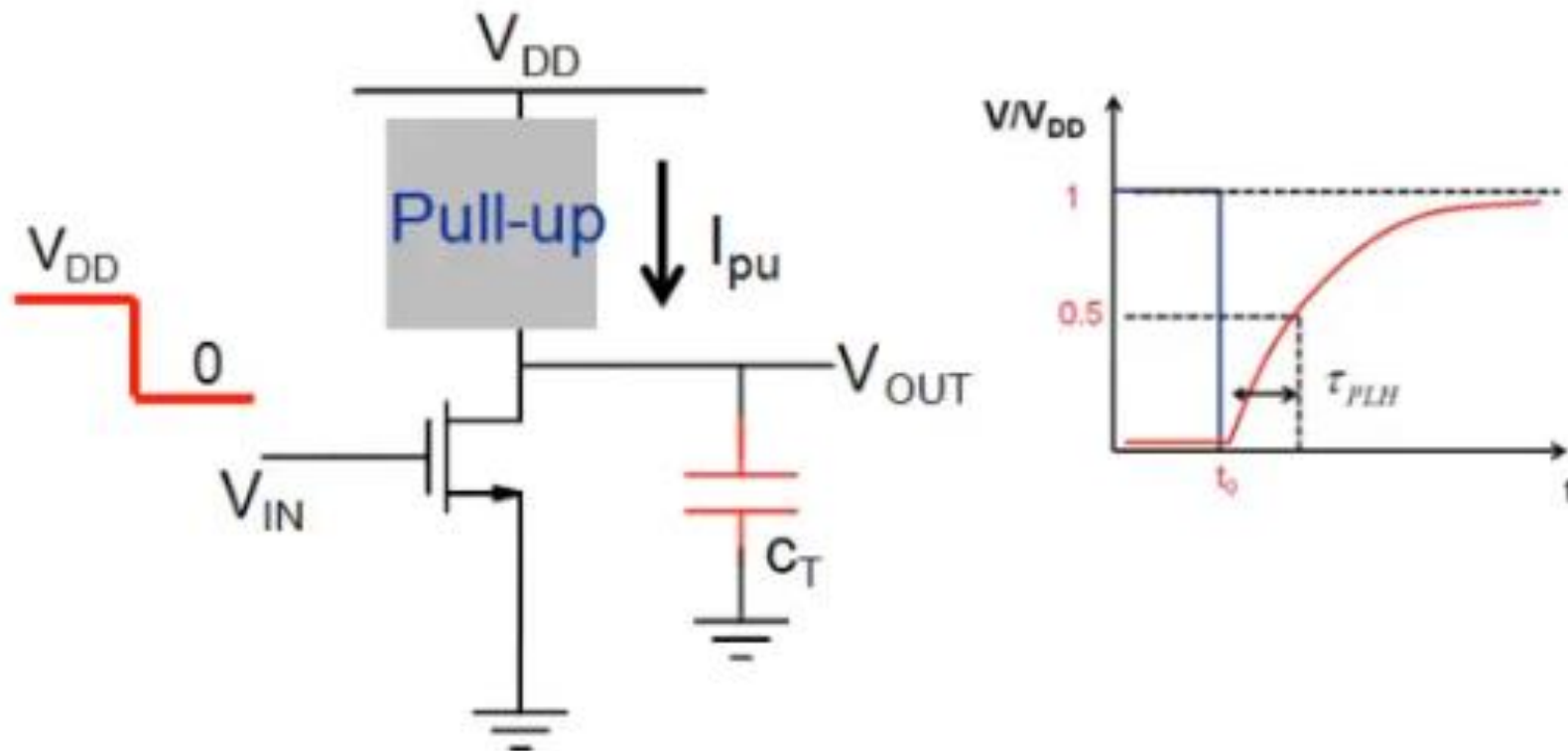
$$\tau_{plh} \cong 0.67 \times R_D \tilde{C}_T$$





$$\tau_{plh} \cong 0.5 \times \frac{\tilde{C}_T V_{DD}}{\tilde{I}_{pu}}$$

$$I_{pu} \propto V_{DD}^m; m > 1 \quad P_{diss} \propto V_{DD}$$


In general delay decreases with increase in supply voltage

There is a power delay tradeoff

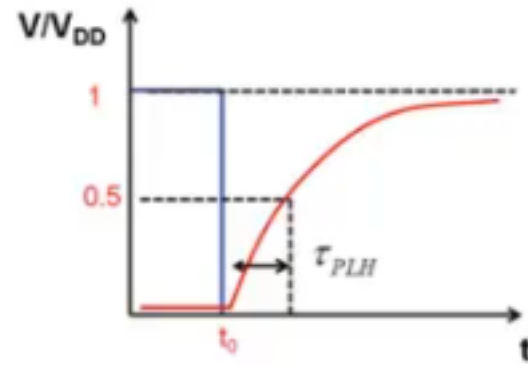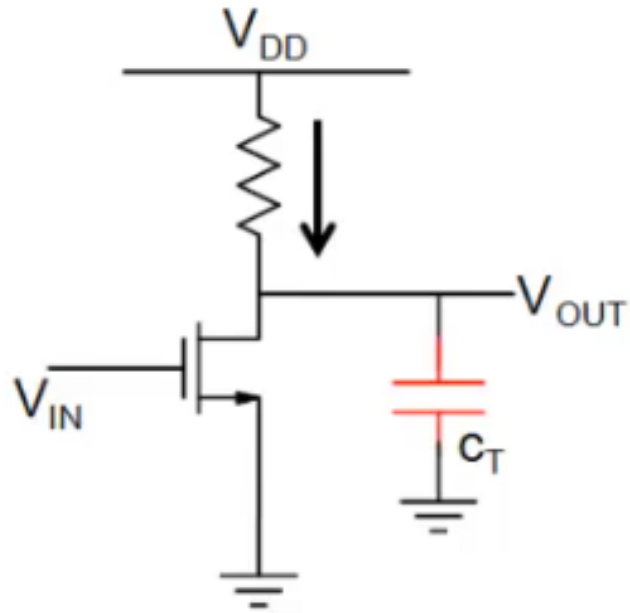


$$I_{pu} = \frac{V_{DD}}{R_D} \rightarrow \frac{0.5V_{DD}}{R_D}$$
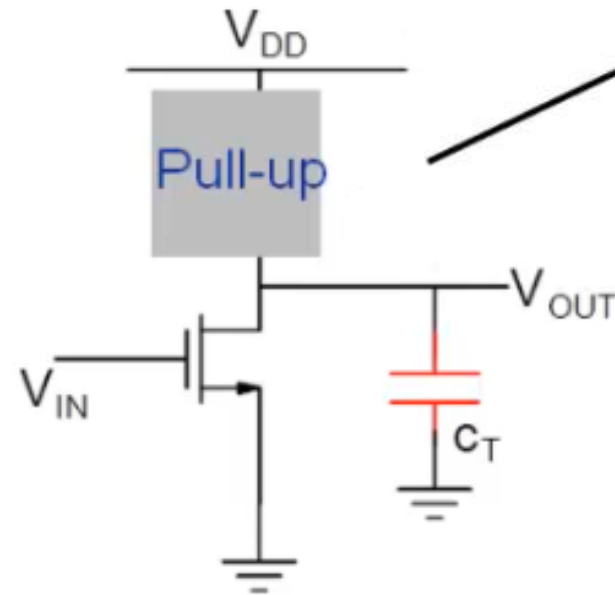
$$\tau_{plh} \cong 0.5 \times \frac{\tilde{C}_T V_{DD}}{\tilde{I}_{pu}}$$




Ideally should be like a **current source** which switches on during charging.

## High to Low delay propagation Delay

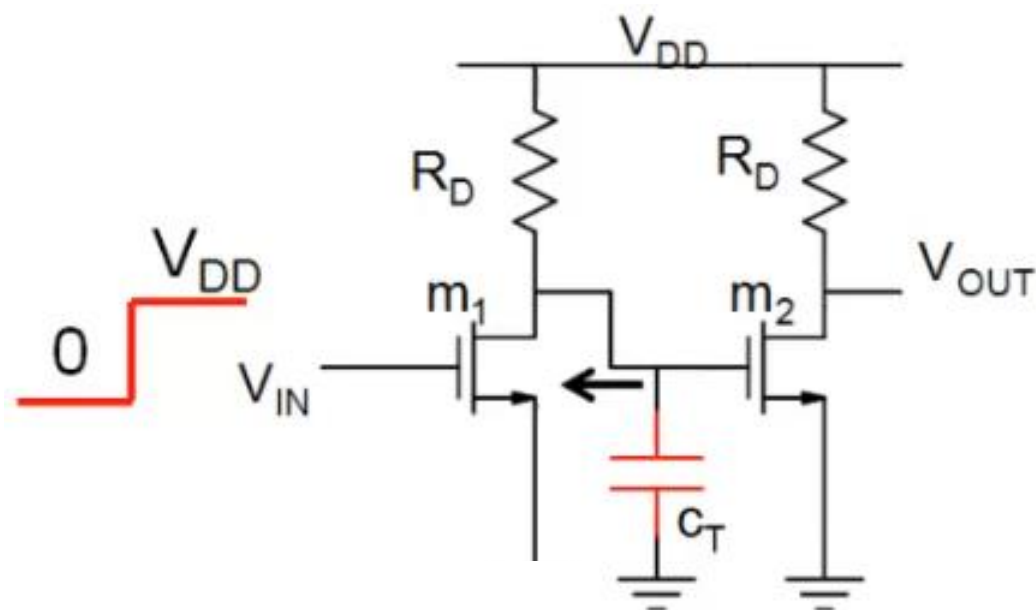

$$\tau_{phl} \cong 0.5 \times \frac{\tilde{C}_T V_{DD}}{\tilde{I}_{dis.}}$$
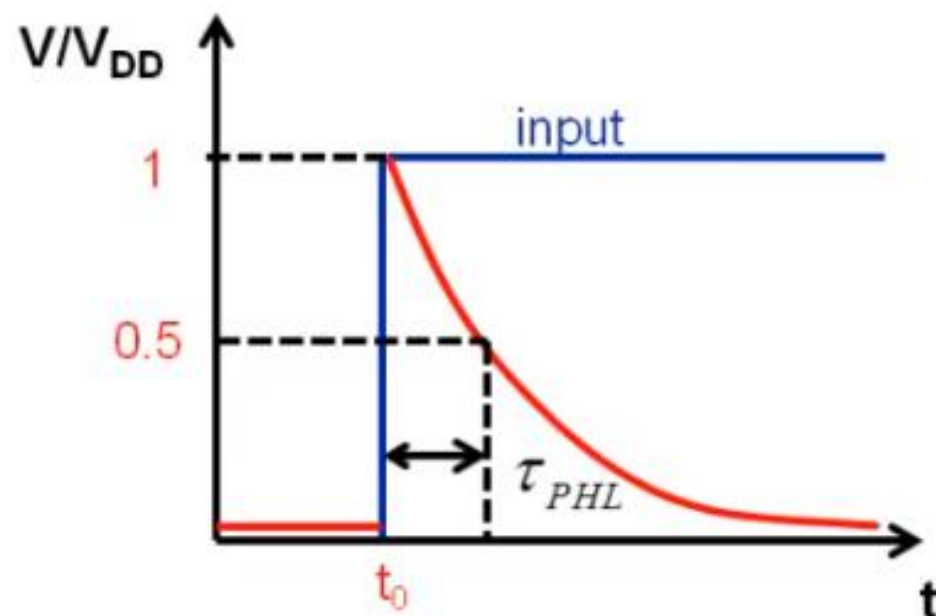
$$I_{dis.} = I_{DS1} - \frac{V_{DD} - V_{D1}}{R_D}$$




M1 : sat (3.3→2.3)  
lin. (2.3→1.65)

$$I_{DS}(t=0) = \left( KP_N \times \frac{W}{L} \right) \times \frac{(V_{DD} - V_{THN})^2}{2}$$

$$I_{DS}(t=\tau_{phl}) = \left( KP_N \times \frac{W}{L} \right) \times \left( (V_{DD} - V_{THN}) \frac{V_{DD}}{2} - \frac{V_{DD}^2}{4} \right) - \frac{V_{DD}}{2R_D}$$

# High to Low delay propagation Delay

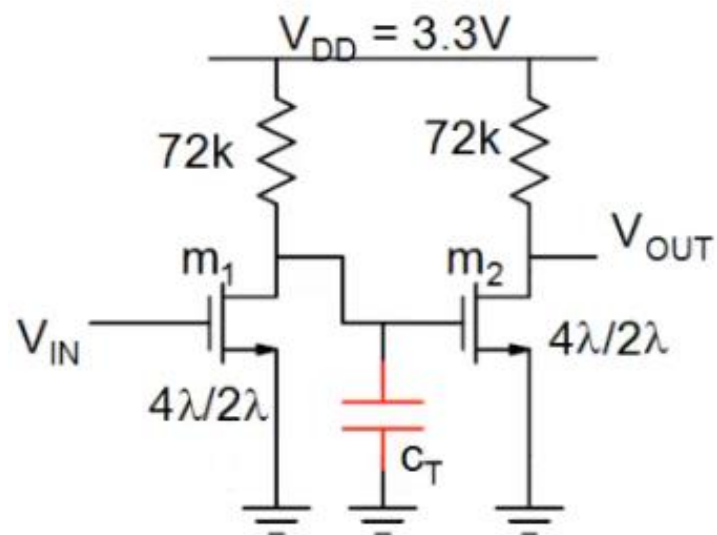


$$\tau_{phl} \cong 0.5 \times \frac{\tilde{C}_T V_{DD}}{\tilde{I}_{dis.}} \sim 39 \text{ ps}$$

$$\tau_{PLH} \cong 424 \text{ ps}$$

$$I_{dis.} = I_{DS1} - \frac{V_{DD} - V_{D1}}{R_D}$$



$$I_{DS}(t=0) = \left( KP_N \times \frac{W}{L} \right) \times \frac{(V_{DD} - V_{THN})^2}{2} \quad 0.53 \text{ mA}$$
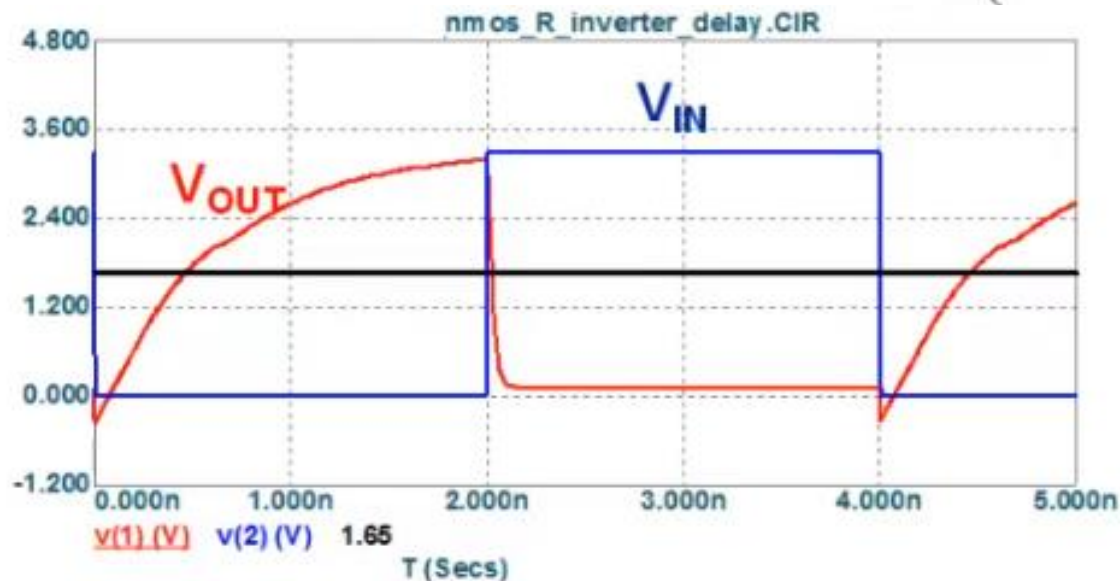
$$I_{DS}(t=\tau_{phl}) = \left( KP_N \times \frac{W}{L} \right) \times \left( (V_{DD} - V_{THN}) \frac{V_{DD}}{2} - \frac{V_{DD}^2}{4} \right) - \frac{V_{DD}}{2R_D} \quad 0.19 \text{ mA}$$







# Power dissipation

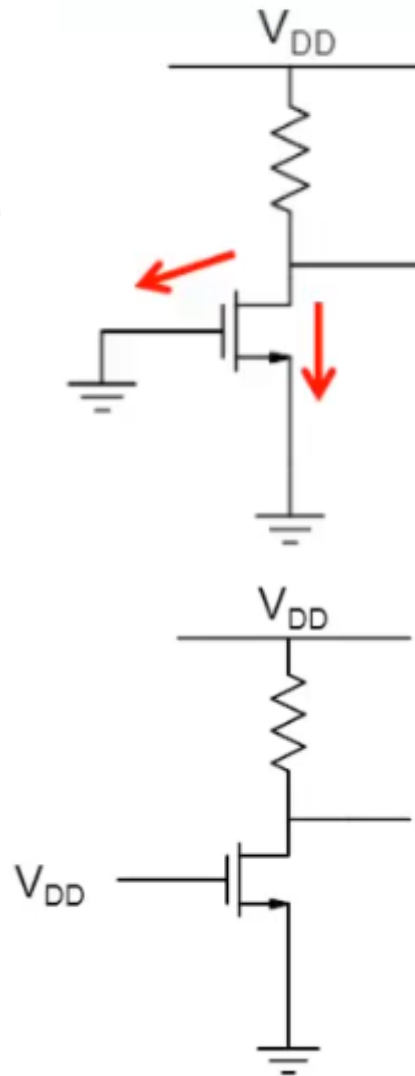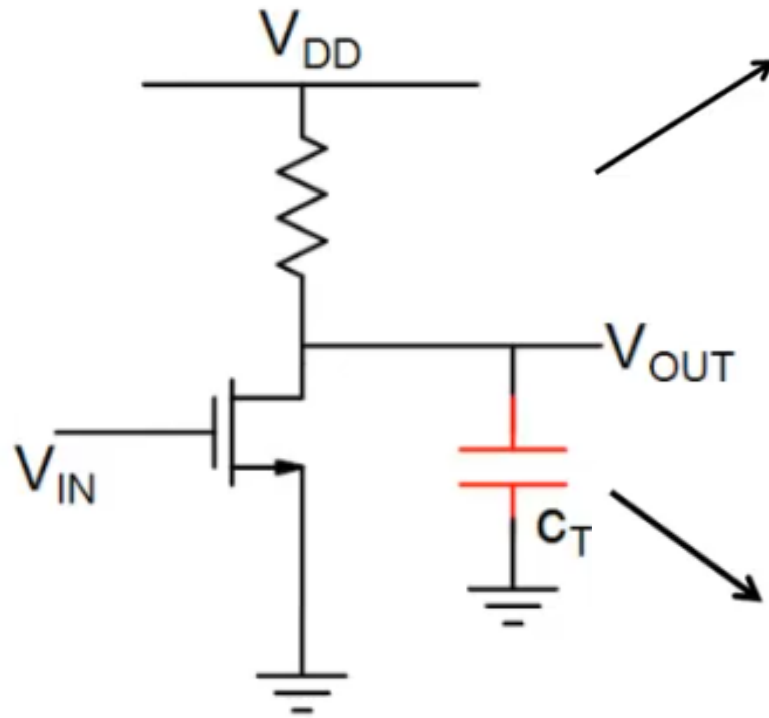

$$P = V_{DD} \times I_{leakage}$$

$$P \sim \frac{V_{DD}^2}{R_D}$$

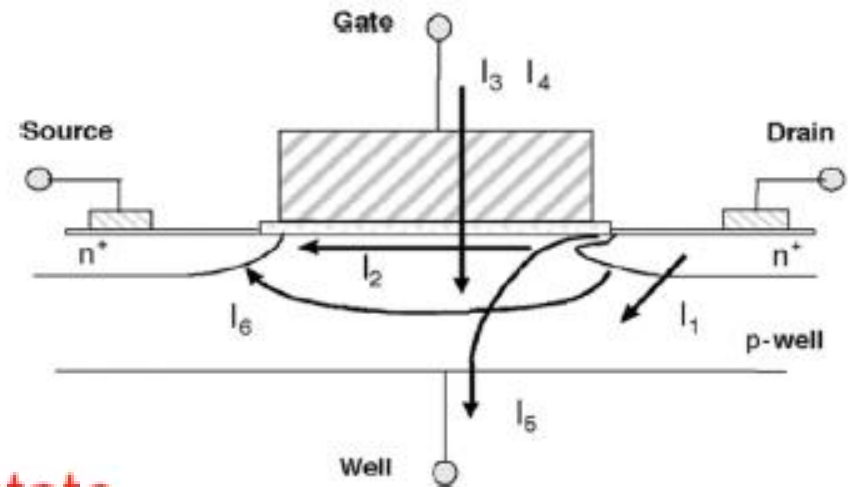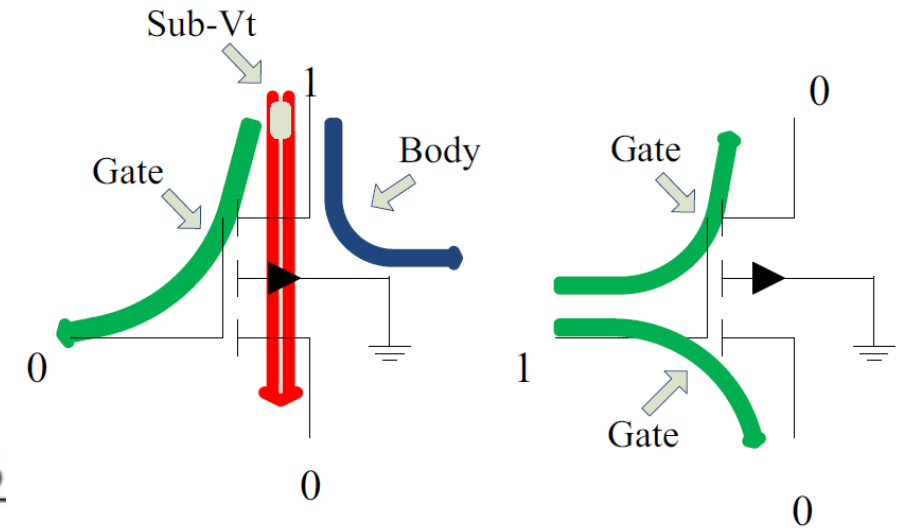

1. Static
2. Dynamic

Energy should be drawn only to change the state

- If channel is **locking**:


- subthreshold current ( $I_{\text{subth}}$ )
- gate tunnelling to S/D ( $I_{\text{gate}}$ )
- pn-junction leakage ( $I_{\text{junction}}$ )
- gate induced drain leakage ( $I_{\text{GIDL}}$ )
- depletion punchthrough ( $I_{\text{punch}}$ )

- If channel is **conducting**:


- gate tunnelling ( $I_{\text{gate}}$ )
- pn-junction leakage ( $I_{\text{junction}}$ )

- If channel is **switching**:



- hot carrier injection ( $I_{\text{HCI}}$ )

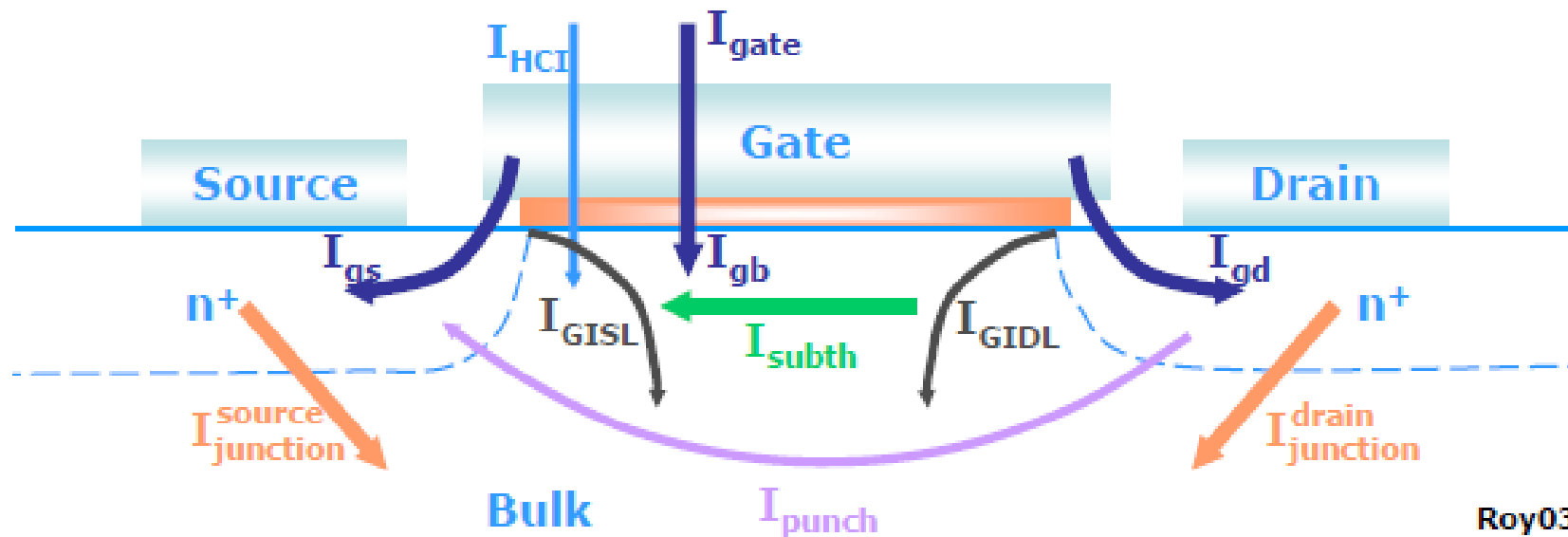

Roy03

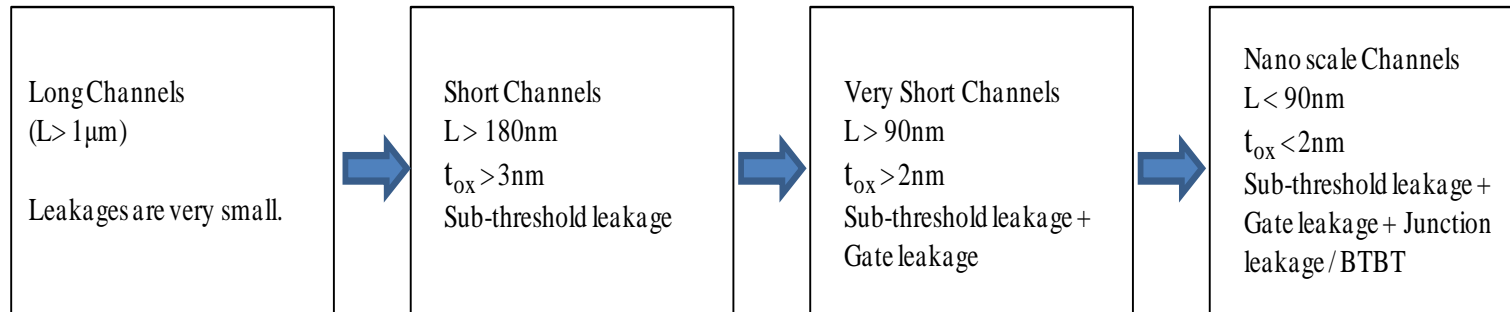

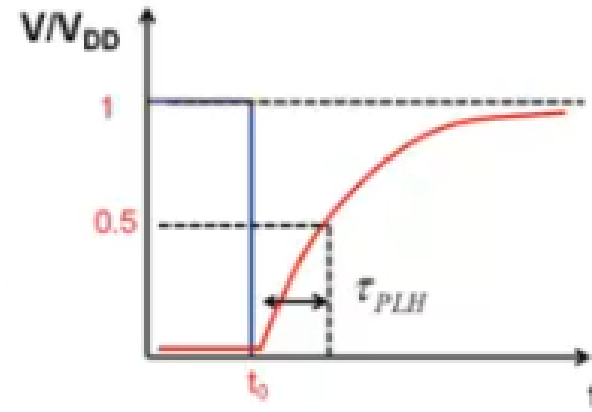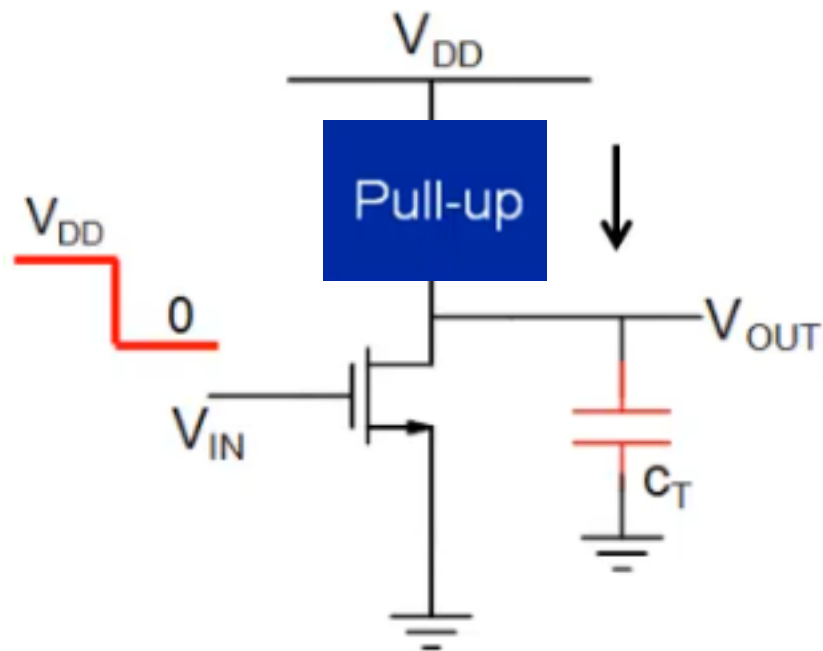
Contribution of new leakage currents with scaled technologies




$$E_{supply} = \int V_{DD} \times I_{pu} dt = C_T \times V_{DD}^2$$

Half of it is dissipated in the resistor and the other half is stored in capacitor


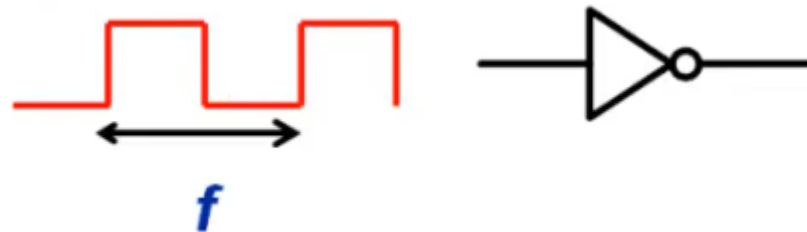
When the inverter switches back to zero, the energy stored on capacitor is also dissipated


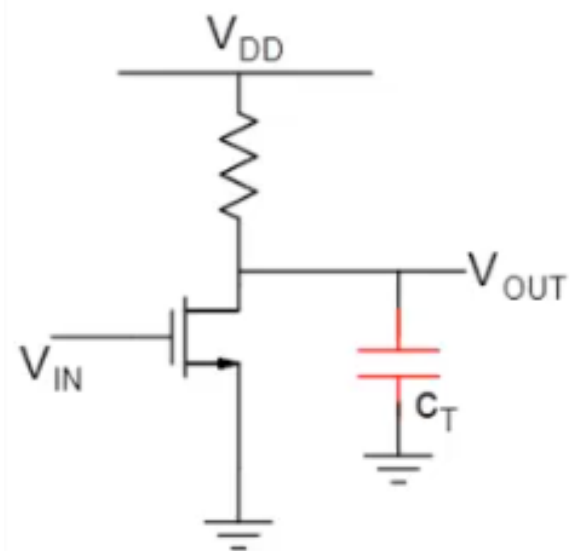
$$P_{dynamic} = \frac{0.5C_T \times V_{DD}^2 + 0.5C_T \times V_{DD}^2}{T} = C_T \times V_{DD}^2 \times f$$


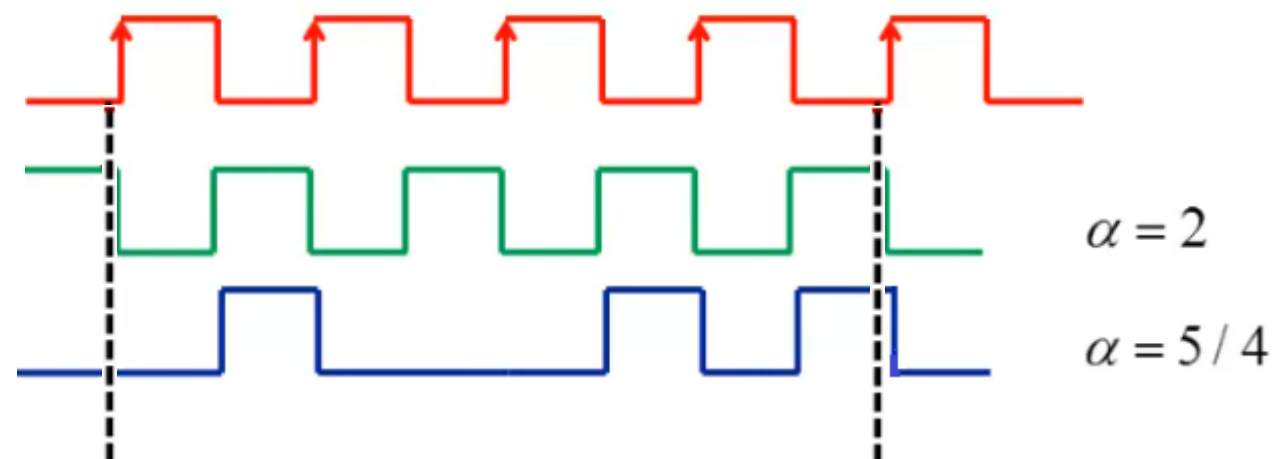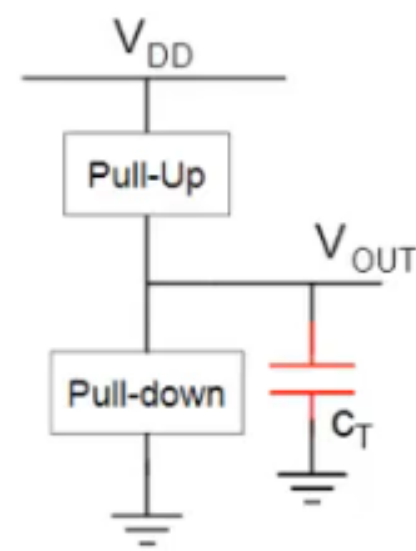
$$P_{dynamic} = C_T \times V_{DD}^2 \times f$$



$$P_{dynamic} = \sum (0.5 C_j \times V_j^2) \times f \times \alpha_j$$